



# V2V EDTECH LLP

Online Coaching at an Affordable Price.

## OUR SERVICES:

- Diploma in All Branches, All Subjects
- Degree in All Branches, All Subjects
- BSCIT / CS
- Professional Courses



**+91 93260 50669**



**v2vedtech.com**



**V2V EdTech LLP**



**v2vedtech**



WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

1

**Important Instructions to examiners:**

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.



Q. No.	Sub Q. N.	Answers	Marking Scheme
1	(A)	Attempt any FIVE of the following:	10- Total Marks
	(a)	Define:  (i) Admittance (ii) Conductance	2M
	Ans:	i) Admittance:-  Admittance is defined as the reciprocal of impedance .It is denoted by Y.  It is given by $Y = (1/Z)$  ii) Conductance:  Conductance is the ratio of resistance to the square of impedance .It is denoted by G.  It is given by $G = (R/Z^2)$	1 M  for each definition

WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

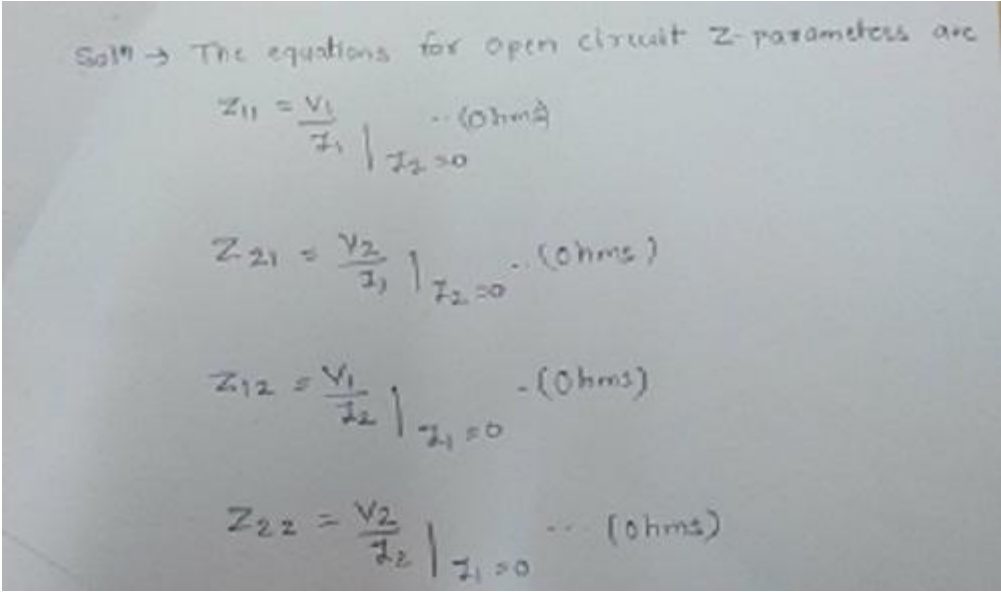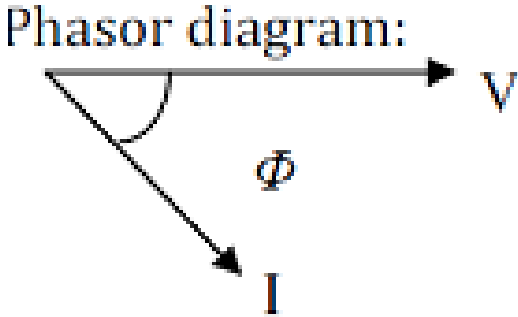(b)	Write the equation of open circuit Z parameter.	2M
Ans:		½M for each equation
(c)	Draw phasor diagram for R-L series circuit.	2M
Ans:	<p>Phasor diagram for R-L series circuit.</p>  <p>(OR)</p>	2M


WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330


3

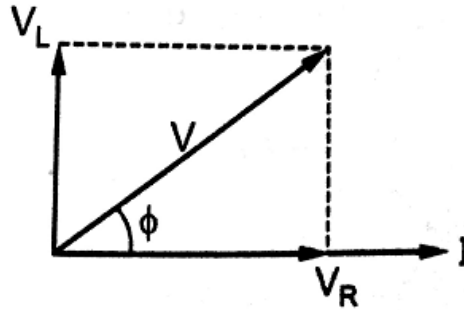

(d) Draw resonance curve for series resonance.

2M

Ans:

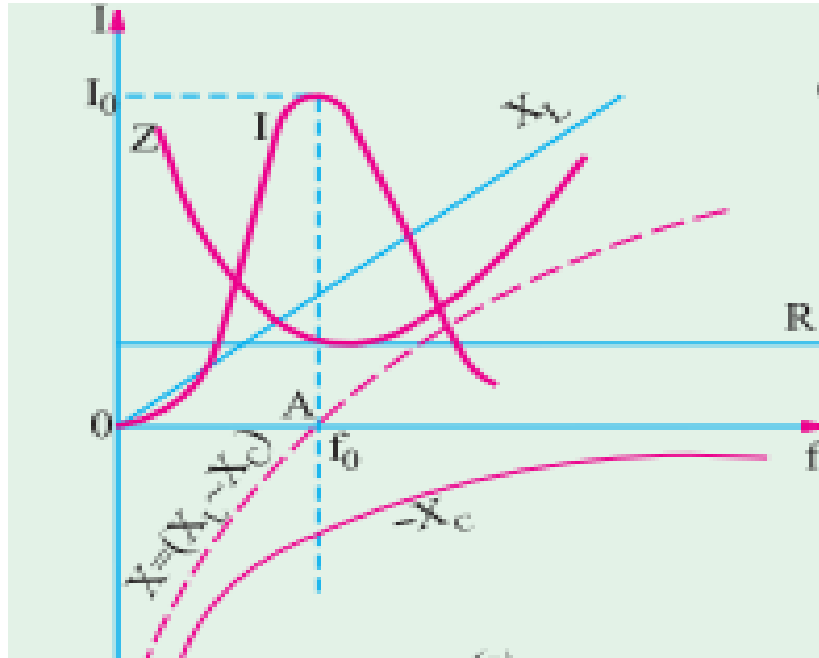

2M

e) Define:

2M

- (i) Node
- (ii) Branch

- Ans:
- i) **Node** : Node is a junction or common point in a network where two or more branches meet.
  - ii) **Branch** : A branch is defined as that part of a network which lies between two junctions.



1 M for each definition

WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

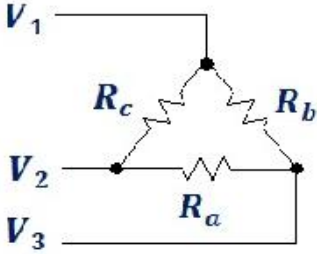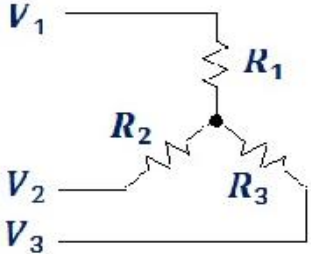f)	State Thevenins theorem.	2M
Ans:	Any network containing active and/or passive elements and one or more dependent and/or independent voltage/or current sources can be replaced by an equivalent network containing a voltage source (Thevenin's equivalent voltage $V_{TH}$ or $V_{OC}$ ) and a series resistance (called Thevenin's equivalent resistance $R_{TH}$ ), where $V_{OC}$ or $V_{Th}$ is the voltage measured across specified open terminals and $R_{Th}$ is the resistance measured across the same terminals when all the sources present in the network are replaced by their internal resistances.	2M
g)	Write the formula for Delta to Star conversion giving examples.	2M
Ans:	<p>The formula for Delta to Star conversion-</p> <div style="display: flex; justify-content: space-around; align-items: center;">   </div> $R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$ $R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$ $R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$	2M

Q. No.	Sub Q. N.	Answers	Marking Scheme
2		Attempt any THREE of the following:	12- Total Marks





WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

5

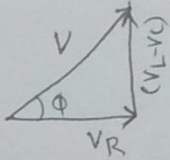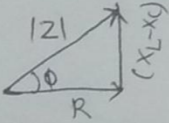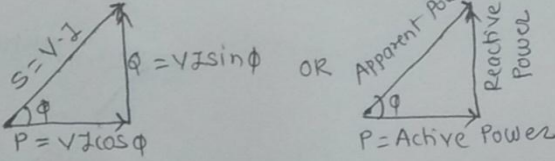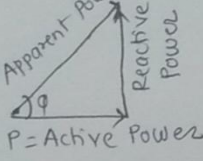a)	For RLC series circuit draw voltage triangle, power triangle and impedance triangle along with proper labellings and equations for condition $V_L > V_C$ .	4M
Ans:	<p>Sol<sup>n</sup> → For R-L-C series circuit (For cond<sup>n</sup> <math>V_L &gt; V_C</math>)</p> <p>i) Voltage Triangle is given by</p>  <p>ii) Impedance Triangle for <math>V_L &gt; V_C</math> is given by</p>  <p>iii) Power Triangle for <math>V_L &gt; V_C</math> is given by</p>  <p>OR</p>  <p>iv) The v<sub>t</sub> and current equations for <math>V_L &gt; V_C</math></p> $v(t) = V_m \sin \omega t$ $i(t) = I_m \sin(\omega t - \phi)$	<p>Voltage triangle- 1 M</p> <p>Impedance triangle- 1M</p> <p>Power triangle -1 M</p> <p>Voltage equation-1/2M</p> <p>Current equation-1/2 M</p>
b)	Define and state equations for (i) Active Power (ii) Reactive Power (iii) Apparent Power.	4M
Ans:	<p>i) Active Power (P):</p> <p>The active power is defined as the average power <math>P_{avg}</math> taken by or consumed by the given</p>	<p>Active power: 1.5 M</p>



WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

6

	<p>circuit.</p> <p style="text-align: center;"><b>(OR)</b></p> <p>It is the power which is actually dissipated in the circuit resistance.</p> <p style="text-align: center;"><math>P = V.I.\cos\phi = I^2R</math></p> <p style="text-align: center;"><b>Unit:</b> - Watt <b>OR</b> Kilowatt</p> <p><b>ii)Reactive Power (Q):-</b></p> <p>It is the power developed in the reactive elements present in the circuit.</p> <p style="text-align: center;"><b>(OR)</b></p> <p>The reactive power is defined as the product of V, I and sine of angle between V and I .</p> <p style="text-align: center;"><math>Q= V.I. \sin\phi</math></p> <p style="text-align: center;"><b>Units:</b> - VAR <b>OR</b> KVAR</p> <p><b>iii)Apparent Power (S):-</b></p> <p>It is the product of rms values of applied voltage and current.</p> <p><b>Unit:</b> volt-ampere (VA) <b>OR</b> kilo-volt-ampere (kVA) <b>OR</b> Mega-volt-ampere (MVA)</p> <p><math>S=VI=I^2Z</math> VA</p>	<p><b>Reactive power</b></p> <p><b>1.5 M</b></p> <p><b>Apparent power:</b></p> <p><b>1 M</b></p>
c)	<p><b>Explain the steps for converting practical voltage source into practical current source.</b></p>	<p><b>4M</b></p>
Ans:		

WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

7

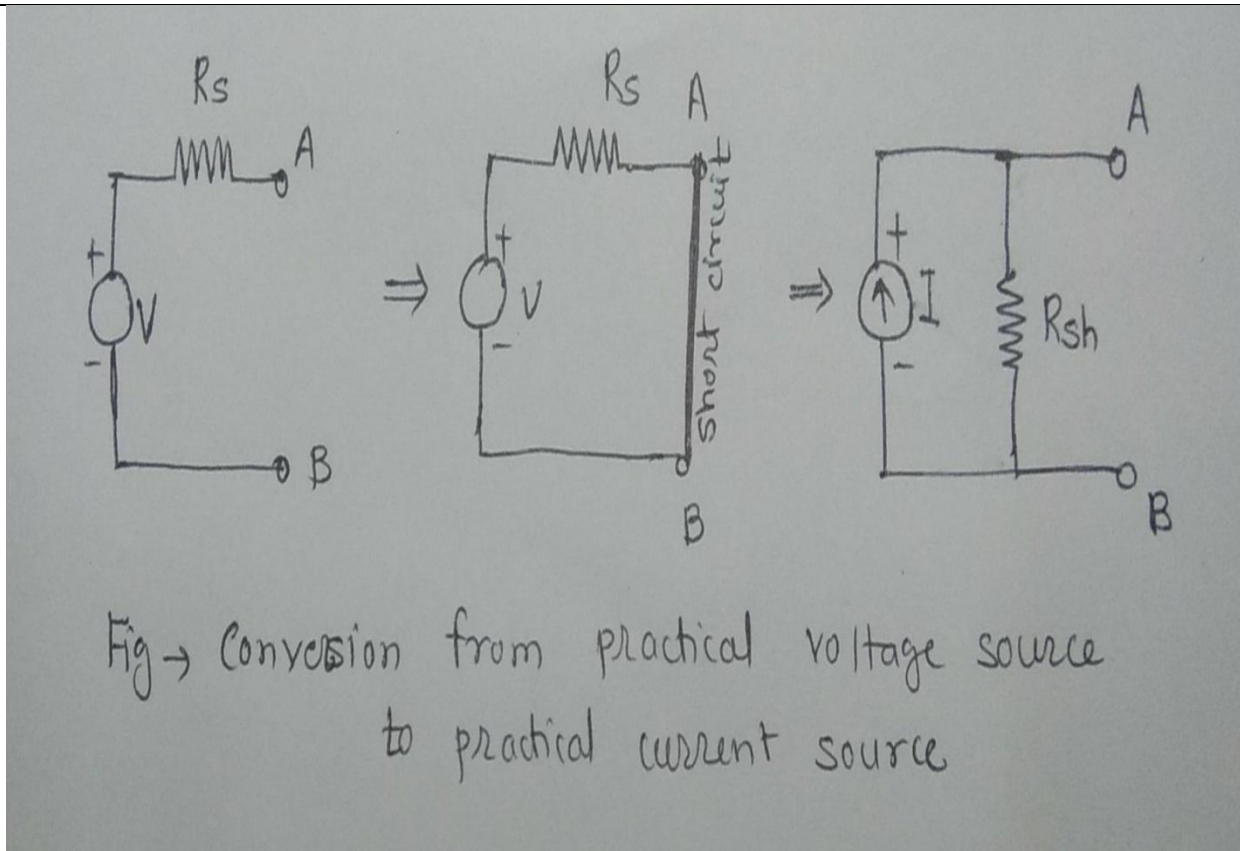


Diagram  
:2 M

A given voltage source with a series resistance can be converted into an equivalent current source with a parallel resistance.

The steps for converting practical voltage source into practical current source are :

i) Terminals A and B of the given voltage source is short circuited as shown. Current supplied by the source is given by

Current  $I = V/R$ .

ii) The value of resistance which is connected in parallel with the equivalent current source will have the same value as that of series resistance. That is  $R_s = R_{sh}$ .

ii) The equivalent current source is connected in parallel with the shunt (parallel) resistance.

Steps  
2 M



WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

8

d) Three resistances  $32 \Omega$ ,  $40 \Omega$ ,  $48 \Omega$  are connected in star circuit. Determine its equivalent delta circuit. **4M**

Ans:

$$R = R_1 R_2 + R_2 R_3 + R_3 R_1$$

$$= (32 \times 40) + (40 \times 48) + (48 \times 32)$$

$$\therefore R = 4736 \Omega$$

Now,

$$R_{12} = \frac{R}{R_3} = \frac{4736}{48} = 98.66 \Omega$$

$$R_{23} = \frac{R}{R_1} = \frac{4736}{32} = 148 \Omega$$

$$R_{31} = \frac{R}{R_2} = \frac{4736}{40} = 118.4 \Omega$$

Q. No.	Sub Q. N.	Answers	Marking Scheme
3		Attempt any THREE of the following :	12- Total Marks

WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

a)	If $Z_1 = 3 + j7$ and $Z_2 = 12 - j16$ are connected in parallel. Find the equivalent impedance of combination.	4M
Ans:	<p>Equivalent impedance, <math>Z_{eq} = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(3+j7)(12-j16)}{(3+j7)+(12-j16)} = \frac{(7.62 \angle 66.8)(20 \angle -53.13)}{(7.62 \angle 66.8) + (20 \angle -53.13)} =</math></p> $= \frac{152.4 \angle 13.67}{17.5 \angle -40} = 8.71 \angle 53.67 = 5.16 + j7 \Omega$	<p>Formula 1M Steps 1M Ans. 2M</p>
b)	Determine Bandwidth and Quality factor (Q) for the series circuit.	4M
Ans:	<p><b>Band width:</b></p> <p>The bandwidth of a series circuit is given by the band of frequencies which lies between two points on either side of <math>f_0</math> where current falls to <math>I_0 / \sqrt{2}</math>. (graph may be desirable)</p> <div data-bbox="558 1121 1089 1612" data-label="Figure"> </div> <p>From the given fig., band width AB is,</p> $AB = \Delta f = f_2 - f_1 \text{ or } AB = \Delta \omega = \omega_2 - \omega_1 \text{ where } f_1 \text{ and } f_2 \text{ are the corner or edge frequencies.}$	<p>2 M each</p>



WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

10

(OR)

$$\Delta f = f_r / Q_r = \frac{1}{\frac{2\pi\sqrt{LC}}{1\sqrt{L}}} = \frac{R}{2\pi L}$$

Quality factor:

Note: any one of the following can be considered

Reciprocal of power factor is called quality ( $Q$ ) factor or its figure of merit. The  $Q$ -factor of a series circuit can be defined as the ratio of impedance to resistance.

$$Q = \frac{Z}{R}$$

It is also defined as,

$$Q = 2\pi \frac{\text{maximum energy stored per cycle}}{\text{Energy dissipated per cycle}}$$

For a resonant circuit it may be determined in any of the following ways

i) It is given by the voltage magnification produced in the circuit at resonance.

$$\begin{aligned} \text{Voltage magnification} &= \frac{V_{L_0}}{V} = \frac{I_0 X_{L_0}}{I_0 R} = \frac{\text{reactive power}}{\text{active power}} = \frac{X_{L_0}}{R} = \frac{\omega_0 L}{R} = \frac{\text{reactance}}{\text{resistance}} \\ \text{or} &= \frac{V_{C_0}}{V} = \frac{I_0 X_{C_0}}{I_0 R} = \frac{\text{reactive power}}{\text{active power}} = \frac{X_{C_0}}{R} = \frac{\text{reactance}}{\text{resistance}} = \frac{1}{\omega_0 CR} \\ \therefore Q\text{-factor, } Q_0 &= \frac{\omega_0 L}{R} = \frac{2\pi f_0 L}{R} = \tan \phi \end{aligned}$$

ii)



WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

11

$$Q\text{-factor} = 2\pi \frac{\text{maximum stored energy}}{\text{energy dissipated per cycle}} \quad \dots \text{in the circuit}$$

$$= 2\pi \frac{\frac{1}{2} LI_0^2}{I^2 R T_0} = 2\pi \frac{\frac{1}{2} L(\sqrt{2}I)^2}{I^2 R (1/f_0)} = \frac{I^2 2\pi f_0 L}{I^2 R} = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 CR} \quad \dots (T_0 = 1/f_0)$$

iii)

resonant frequency,  $f_0 = \frac{1}{2\pi\sqrt{LC}}$  or  $2\pi f_0 = \frac{1}{\sqrt{LC}}$

Substituting the above in equation,  $Q_0 = \frac{2\pi f_0 L}{R}$ , we get,

$$Q_0 = \frac{1}{R} \sqrt{\frac{L}{C}}$$

iv)  $Q$ -factor of a resonant series circuit may be written as,

$$Q_0 = \frac{\omega_0}{\text{bandwidth}} = \frac{\omega_0}{\Delta\omega} = \frac{\omega_0}{R/L} = \frac{\omega_0 L}{R} = \frac{L}{R\sqrt{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

v) It may also be deduced as,

$$Q_0 = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} = \frac{1}{R} \sqrt{\frac{L}{C}} = \sqrt{\frac{X_{L0} X_{C0}}{R}} = \frac{f_0}{B_{hp}} = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{f_0}{f_2 - f_1}$$

Where  $B_{hp}$  = bandwidth of the circuit



WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

12

c) Using Mesh Analysis find current through  $4\ \Omega$  resistance.(Refer fig. 1)

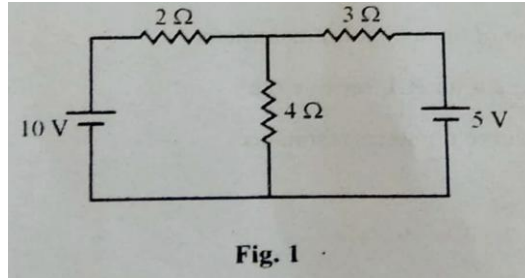


Fig. 1

4M

WINTER- 18 EXAMINATION


Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

13

Ans:

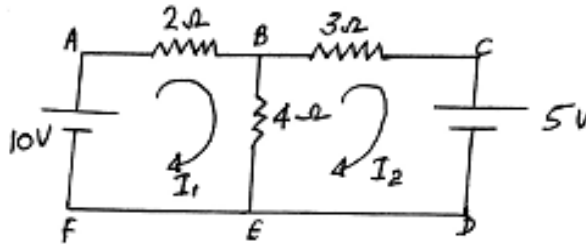

① Apply KVL to loop ABEFA,

$$-2I_1 - 4(I_1 - I_2) + 10 = 0$$

$$-2I_1 - 4I_1 + 4I_2 = -10$$

$$-6I_1 + 4I_2 = -10 \quad \text{--- ①}$$

② Apply KVL to loop BCDEB,

$$-3I_2 - 5 - 4(I_2 - I_1) = 0$$

$$-3I_2 - 5 - 4I_2 + 4I_1 = 0$$

$$4I_1 - 7I_2 = 5 \quad \text{--- ②}$$

Solving eqns ① & ② we get,

$$I_1 = 1.92 \text{ A}, \quad I_2 = 0.38 \text{ A}$$

$$\therefore \text{Current through } 4\Omega, \quad I_1 - I_2 = 1.92 - 0.38 = 1.54 \text{ A (downwards)}$$

Correct  
calculati  
on-  
4M(Give  
step  
marking  
)

d)

Explain the procedure for solving Thevenin's theorem using suitable example.

4M

Ans:

Steps to find Thevenin's equivalent circuit, taking an example is as follows:

1M each

WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

14

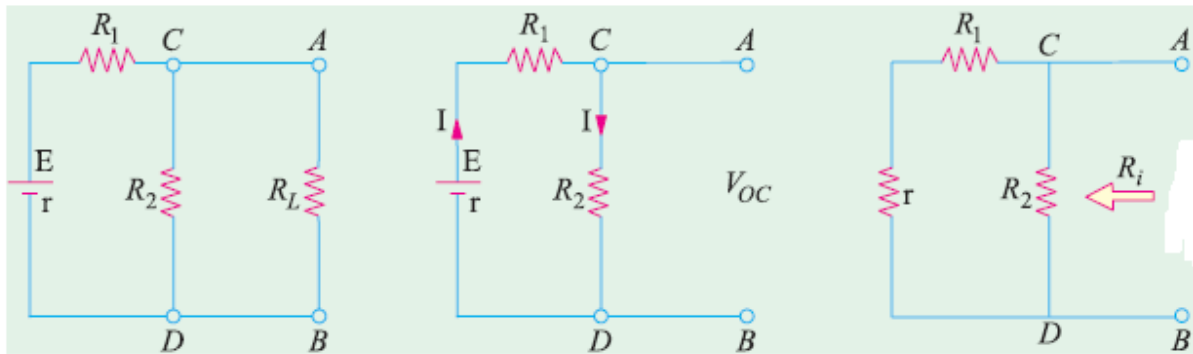


Fig.(a)

fig.(b)

fig.(c)

1. From the given circuit(fig.a), Remove  $R_L$  from the terminals  $A$  and  $B$  and redraw the circuit as shown in Fig.b.

2. Calculate the open-circuit voltage  $V_{oc}$  which appears across terminals  $A$  and  $B$ .

As seen,  $V_{oc} = \text{drop across } R_2 = IR_2$  where  $I$  is the circuit current when  $A$  and  $B$  are open.

$$I = \frac{E}{R_1 + R_2 + r} \quad \therefore V_{oc} = IR_2 = \frac{ER_2}{R_1 + R_2 + r} \quad [r \text{ is the internal resistance of battery}]$$

It is also called 'Thevenin voltage'  $V_{th}$ .

3. Now, imagine the battery to be removed from the circuit, leaving its internal resistance  $r$  behind and redraw the circuit, as shown in Fig.(c). When viewed *inwards* from terminals  $A$  and  $B$ , the equivalent resistance is given as,

$$R = R_2 \parallel (R_1 + r) = \frac{R_2(R_1 + r)}{R_2 + (R_1 + r)}$$

This is called Thevenin's equivalent resistance  $R_{th}$ .

4. Connect  $R_L$  back across terminals  $A$  and  $B$ (fig.d) from where it was temporarily removed earlier.

WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

15

Current flowing through  $R_L$  is given by

$$I = \frac{V_{th}}{R_{th} + R_L}$$

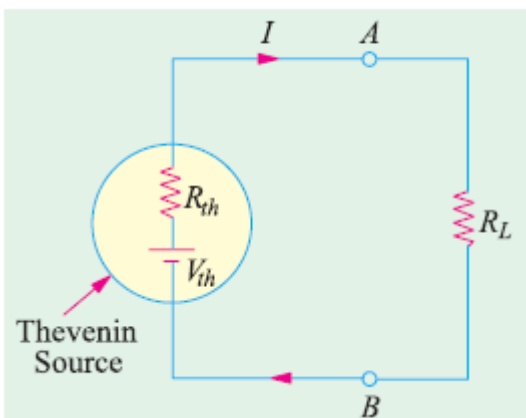


Fig.(d)

Q. No.	Sub Q. N.	Answers	Marking Scheme
4		Attempt any THREE of the following :	12- Total Marks
	(a)	A coil has resistance of $4 \Omega$ and an inductance of 9.55 mH. Calculate (i) Reactance (ii) The impedance (iii) The current taken from 240 V, 50 Hz supply.	4M





WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

16
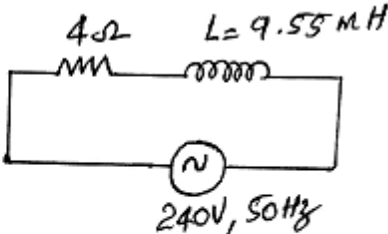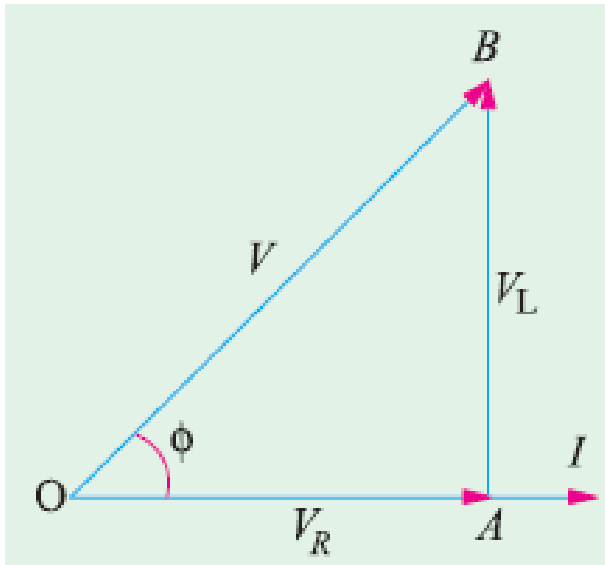
<p>Ans:</p>	 <p>Data given:</p> <p><math>R = 4\Omega</math>, <math>L = 9.55\text{ mA}</math>, <math>V = 240\text{V}</math>, <math>f = 50\text{ Hz}</math></p> <p>i) Reactance, <math>X_L = 2\pi fL = 2 \times 3.14 \times 50 \times 9.55 \times 10^{-3} = 3\Omega</math></p> <p>ii) Impedance, <math>Z = R + jX_L = 4 + j3 = 5 \angle 36.87^\circ \Omega</math></p> <p>iii) Current, <math>I = \frac{V}{Z} = \frac{240}{5} = \underline{\underline{48\text{ A}}}</math></p> <p>(or)</p> <p>ii) Impedance, <math>Z = \sqrt{R^2 + X_L^2} = \sqrt{4^2 + 3^2} = \underline{\underline{5\Omega}}</math></p>	<p>1M each for parameters &amp; 1M for proper steps followed</p>
<p>(b)</p>	<p>Draw the phasor diagrams for a series RL and series RC with AC supply.</p>	<p>4M</p>
<p>Ans:</p>	<p>Phasor diagram of RL series circuit:</p> 	<p>2M for each diagram</p>

WINTER- 18 EXAMINATION


Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

17

Phasor diagram of RC series circuit:

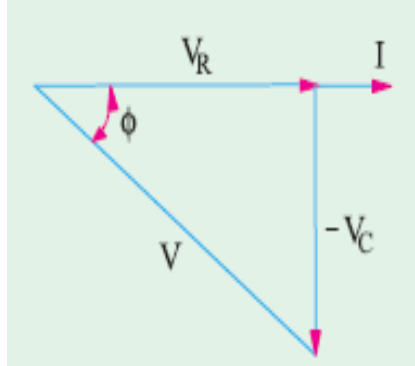

(c) Compare series and parallel circuits.

4M

Ans:

1M each  
for any 4  
points

Sr.No.	Series circuit	Parallel circuit
1	<p>Element are connected end-on-end</p>	<p>Equi-potential ends are connected together</p>
2	<p>Same current flows through all parts of the circuit.</p>	<p>Same voltage acts across all parts of the circuit</p>
3	<p>Different resistors have their individual voltage drops.</p>	<p>Different resistors have their individual currents.</p>
4	<p>Voltage drops are additive.</p>	<p>Branch currents are additive.</p>




WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:


22330

18

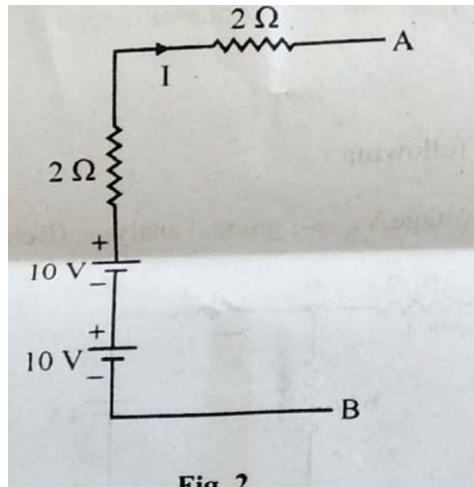
	5	Applied voltage equals the sum of different voltage drops.	Individual voltages is equal to supply voltage	
	6	Resistances are additive.	Conductances are additive.	
	7	Powers are additive.	Powers are additive	
(d)	<p>Using source transformation technique find the resultant current (I) through circuit. (Refer fig. 2)</p>  <p style="text-align: center;">Fig. 2</p>			4M

Ans:

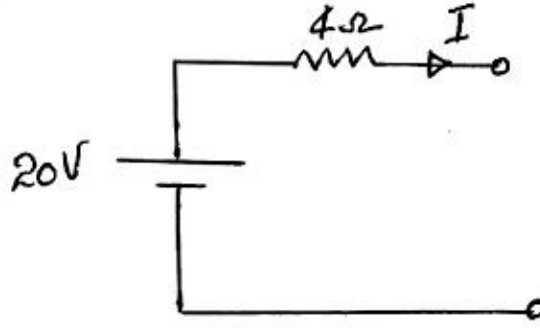Adding both the sources the circuit becomes,



Its equivalent current source is

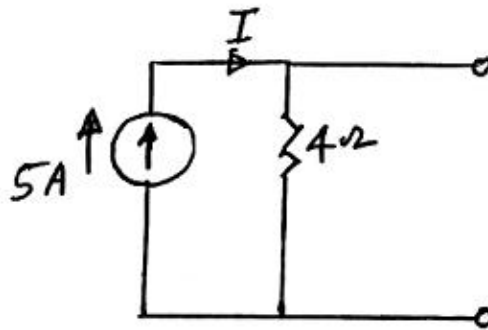

$$I = 5A$$

Correct  
calculati  
on-4M

(e) Using super-position theorem find current through  $4\ \Omega$  resistance. (Refer fig. 3)

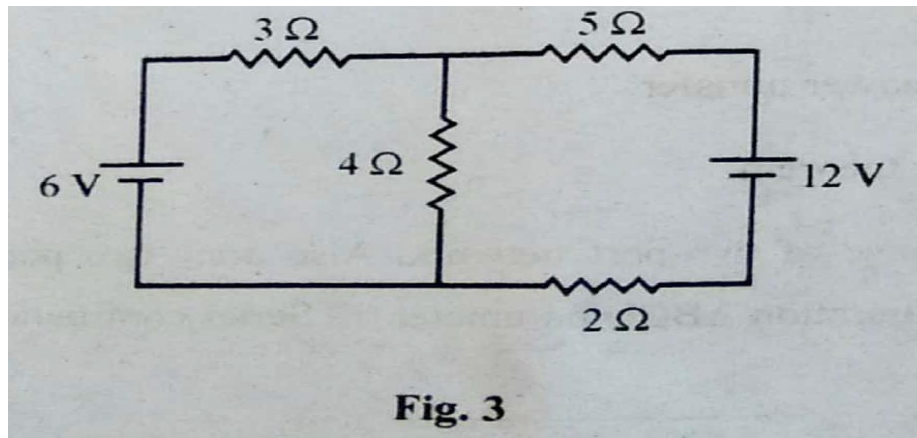


Fig. 3

4M





WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

20

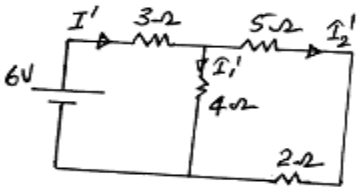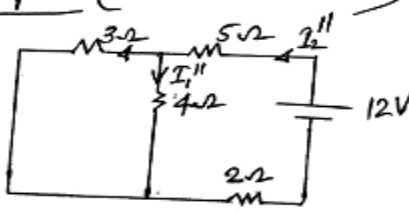Ans:	<p><u>Step I (With 6V source alone)</u></p>  $I = \frac{V}{R_{eq}} = \frac{6}{3 + 4 \parallel (5+2)}$ $= \frac{6}{3 + 2.55} = 1.08 A$ $I_1' = \frac{I' \times (5+2)}{4+5+2} = \frac{1.08 \times 7}{11} = 0.69 A \downarrow$ <p><u>Step II (With 12V alone)</u></p>  $I_2'' = \frac{V}{R_{eq}} = \frac{12}{5 + (3 \parallel 4) + 2}$ $= \frac{12}{8.71} = 1.38 A$ $I_1'' = \frac{I_2'' \times 3}{3+4} = \frac{1.38 \times 3}{7} = 0.59 A \downarrow$ <p>∴ Current through 4Ω = <math>I_1' + I_1'' = 0.69 + 0.59 = 1.28 A \downarrow</math></p>	Corrct calculati on -4M
------	---	-------------------------------

Q. No.	Sub Q. N.	Answers	Marking Scheme
5.		Attempt any TWO of the following:	12- Total Marks
	a)	Derive the expression for resonance frequency for parallel circuit.	6M
	Ans:	A parallel circuit containing an inductance and a capacitance is said to be in resonance when the current through the parallel combination is in phase with the supply voltage.  Consider a parallel combination of L and C as shown below.	Diagram 2M,  derivati on 4M



WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

21

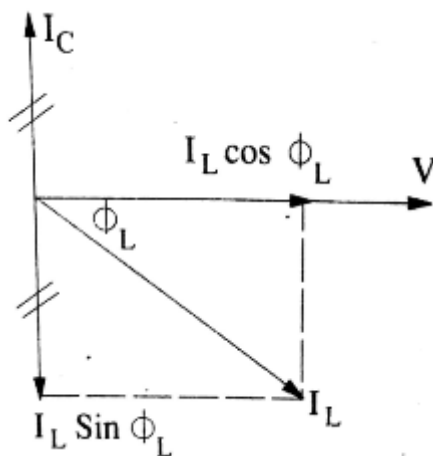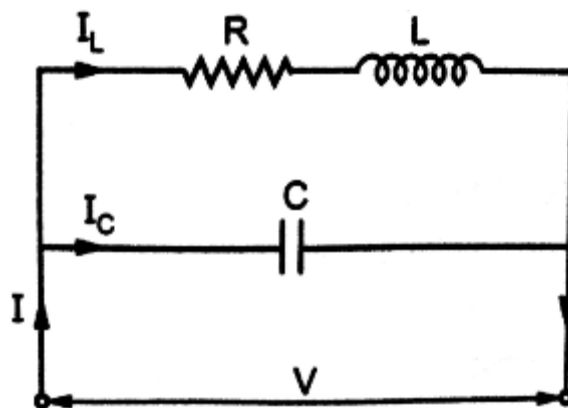

The vector diagram for this circuit is as shown.

The net reactive component of current =  $I_C - I_L \sin \phi_L$ .

At resonance ,its value is zero.

That is  $I_C - I_L \sin \phi_L = 0$  or  $I_C = I_L \sin \phi_L$



WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

22

From the diagram above,  $I_L = V/Z$ ,

$$\sin\phi_L = X_L/Z, I_c = V/ X_c$$

Substituting these values in the above equation, the condition for resonance becomes

$$V/ X_c = (V/Z)( X_L/Z) \text{ or } (X_L)(X_c) = Z^2$$

Substituting  $X_L = \omega L$  and  $X_c = 1/\omega C$

$$(\omega L/ \omega C) = Z^2$$

$$L/C = R^2 + (2\pi fL)^2$$

$$(2\pi fL)^2 = \frac{L}{C} - \frac{R^2}{L^2}$$

$$2\pi f = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

If  $f = f_r$  = resonant frequency, then,

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

If R is negligible, then

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

b) Calculate current through 8 Ω resistance using Norton's theorem.( Refer fig. 4)

6M


WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network


Model Answer Subject Code:

22330

23

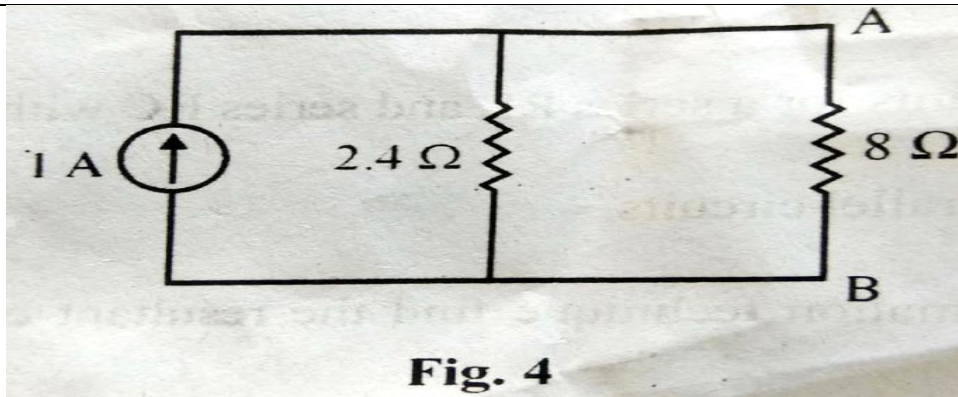

Ans:

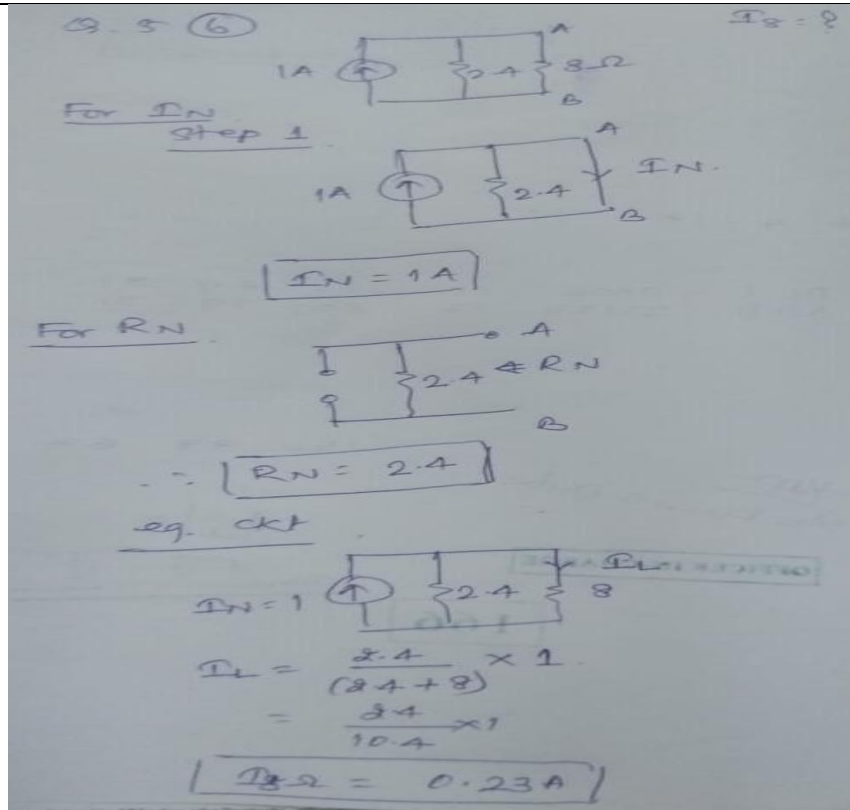

To find

$I_N$  1M

$R_N$  2M

Equivalent ckt.

1M

$I_L$  1M

$I_8$  1M

c) Explain 'Π' and 'T' circuit with proper phasor diagram.

6M

Ans: Note : As phasor diagram of 'Π' and 'T' circuit is not specified in syllabus, marks may be awarded for any relevant diagram and explanation of T and π network.

Diagram 2M each  
Explanation: 1M each



WINTER- 18 EXAMINATION


Subject Name: Electric circuits and network

Model Answer Subject Code:

22330


T networks are used to represent the equivalent of transmission line theory, filters, etc. Ladder network in transmission lines is constructed using T network in series. If Z parameters and ABCD parameters of a network are known, then T network can be constructed.

**T network**

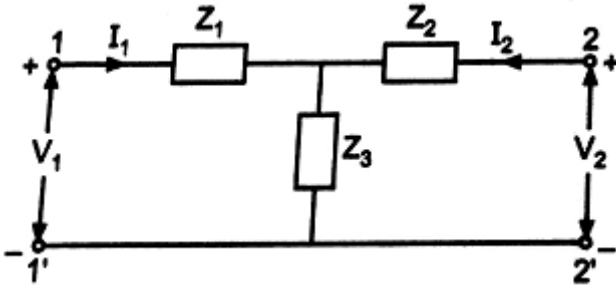

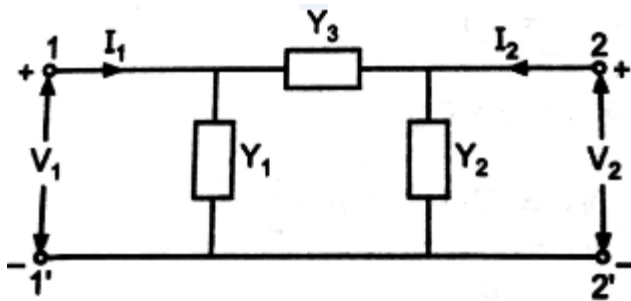**$\pi$  network**

This is also an important network frequently used in transmission line theory. If Y parameters of a network are known, then  $\pi$  network can be constructed.



Q. No.	Sub Q. N.	Answers	Marking Scheme
6.		Attempt any TWO of the following :	12- Total Marks

WINTER- 18 EXAMINATION


Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

25

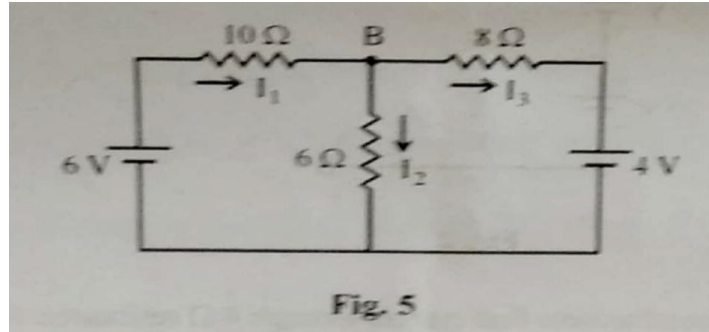a) Calculate the nodal voltage  $V_B$  using nodal analysis. (Refer fig. 5)



6M

Ans:

Q. 6  
②

KCL at 'B'

$$I_1 = I_2 + I_3$$

$$\frac{6 - V_B}{10} = \frac{V_B}{6} + \frac{V_B - 4}{8}$$

$$\frac{6 - V_B}{5} = \frac{4V_B + 3V_B - 12}{12}$$

$$\frac{6 - V_B}{5} = \frac{7V_B - 12}{12}$$

$$72 - 12V_B = 35V_B - 60$$

$$72 + 60 = 35V_B + 12V_B$$

$$132 = 47V_B$$

$$\therefore V_B = \frac{132}{47}$$

$V_B = 2.80V$

Correct  
calculati  
on-6M

b) State and explain:

- (i) Maximum power transfer
- (ii) Reciprocity theorem

6M

Ans: Maximum Power Transfer Theorem:

Maximum Power Transfer Theorem states that "Maximum power is transferred from the

State  
ment 1M

WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network


Model Answer Subject Code:

22330

26

source to the load when the load resistance is equal to the Thevenin's equivalent resistance of the given circuit as seen from load terminals"

i.e,  $R_L = R_{TH}$

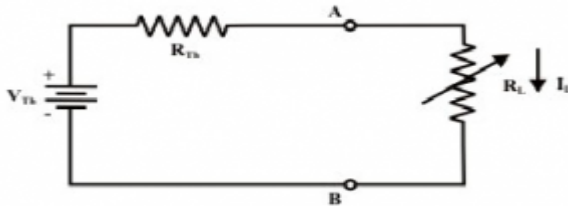

In above figure a variable load resistance  $R_L$  is connected to an equivalent Thevenin circuit of original circuit. The current for any value of load resistance is,

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

Then, the power delivered to the load is..

$$P_L = I_L^2 \times R_L \therefore P_L = \left( \frac{V_{TH}}{R_{TH} + R_L} \right)^2 \times R_L$$

Maximum power transfer occurs when the load resistance  $R_L = R_{TH}$ .

Substituting  $R_L = R_{TH}$  in the above equation, we get

$$P_L = \left[ \frac{V_{TH}}{R_L + R_L} \right]^2 R_L$$

$$= \left( \frac{V_{TH}}{2R_L} \right)^2 \times R_L$$

$$P_{Lmax} = \frac{V^2}{4R_L}$$

**Reciprocity Theorem :**

Statement:

In any linear bilateral network, if a source of emf  $E$  in any branch produces a current  $I$  in any other branch, then the same emf  $E$  acting in the second branch would produce the same current  $I$  in the first branch.

(OR)

each  
Explanat  
ion  
2M each

WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:


22330

27

In any branch of a network or circuit, the current due to a single source of voltage (V) in the network is equal to the current through that branch in which the source was originally placed when the source is again put in the branch in which the current was originally obtained.

Explanation :

Consider the two circuits shown below.

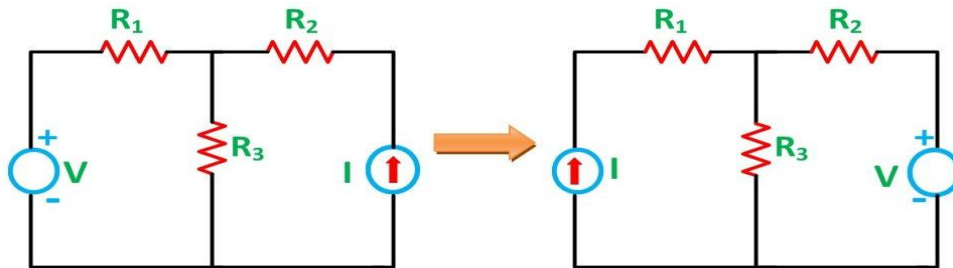

The various resistances  $R_1$ ,  $R_2$ ,  $R_3$  are connected in the circuit diagram above with a voltage source (V) in first loop and an ammeter in second loop in first circuit.

In the second circuit the positions of voltage source and ammeter are interchanged

According to Reciprocity Theorem, the ratio of  $V / I$  called transfer resistance. It remains same in both cases. In this way the theorem is useful for solving networks.

c) Explain significance of two-port network. Also draw two port network for  
(i) Cascade configuration ABCD parameter (ii) Series configuration

6M

Ans: Significance of two-port network:-

2M

A two-port network is regarded as a "black box" with its properties specified by a matrix of numbers. This allows the response of the network to signals applied to the ports to be calculated easily, without solving for all the internal voltages and currents in the network.

2M

Cascade configuration ABCD parameter :-


WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network


Model Answer Subject Code:

22330


2M

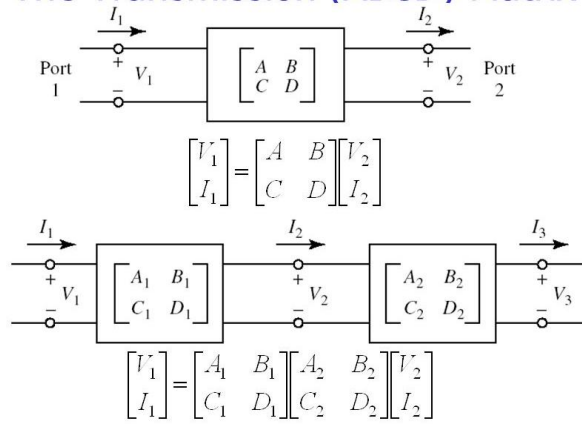


OR

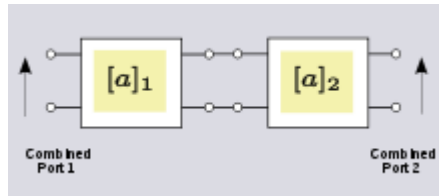

Series configuration:-

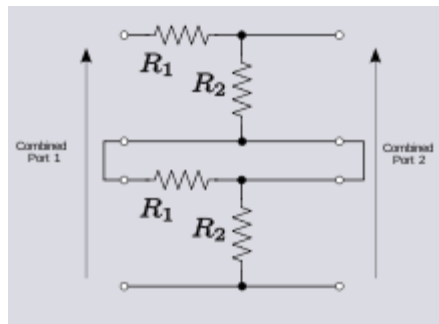

OR

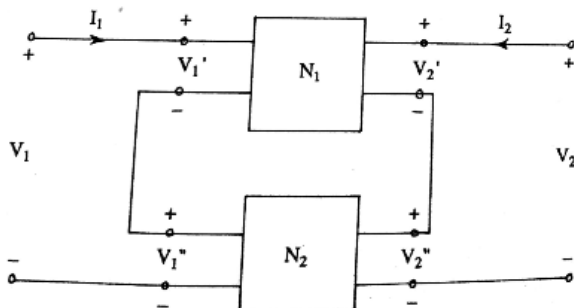



WINTER- 18 EXAMINATION

Subject Name: Electric circuits and network

Model Answer Subject Code:

22330

29

	Where $N_1$ and $N_2$ are two 2-port networks	
--	---	--



# V2V EDTECH LLP

Online Coaching at an Affordable Price.

## OUR SERVICES:

- Diploma in All Branches, All Subjects
- Degree in All Branches, All Subjects
- BSCIT / CS
- Professional Courses



**+91 93260 50669**



**v2vedtech.com**



**V2V EdTech LLP**



**v2vedtech**



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: **22330**

1

**Important Instructions to examiners:**

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q. N.	Answers	Marking Scheme
1	(A)	<b>Attempt any FIVE of the following :</b>	<b>10- Total Marks</b>
	(a)	<b>Define impedance and reactance related to single phase AC series circuit. Give unit of both.</b>	<b>2M</b>
	Ans:	Impedance of single phase AC series circuit is defined as the net opposition offered to the flow of AC current by the combination of R, L and C. Unit of Impedance is $\Omega$ (Ohm). Reactance of single phase AC series circuit is defined as the opposition offered to the flow of AC current by either inductor(L) or capacitor(C). Unit of reactance is $\Omega$ (Ohm).	Each correct definition with its unit- 1M
	(b)	<b>Draw the impedance triangle for R-L series circuit.</b>	<b>2M</b>




SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

2
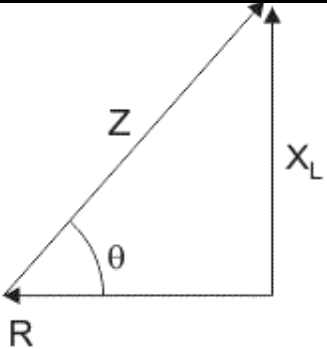
<b>Ans:</b>	 <p><b>Fig. impedance triangle for R-L series circuit.</b></p>	impedance triangle-2M
<b>(c)</b>	<b>State Q factor for parallel R.L.C. circuit.</b>	<b>2M</b>
<b>Ans:</b>	<p>Q factor for parallel R.L.C. circuit is defined as the current magnification provided at resonance. The magnitude of current flowing through inductor and capacitor is equal to Q times the input sinusoidal current I.</p> <p>As the parallel circuit magnifies the current it is also called as the current resonance circuit.</p> <p>OR</p> <p>The Quality factor of Parallel resonance RLC circuit is defined as the ratio of current circulating between its two branches to the line current drawn from the supply.</p> <p>Mathematically, <math>Q = R X_c</math></p>	Any correct definition-2M
<b>(d)</b>	<b>Give four steps to solve nodal analysis.</b>	<b>2M</b>
<b>Ans:</b>	<p>four steps to solve nodal analysis-</p> <ol style="list-style-type: none"> <li>1.all the nodes present in the network including the reference(ground) node)are identified and marked . The number of equations to be solved is given by (n-1) where n= no of independent nodes.</li> <li>2. Mark all the branch currents.</li> <li>3. Using KCL write current equation for each node in terms of node voltage and sources present.</li> <li>4. The equations can be solved either simultaneously or by Cramer's rule to obtain various node voltages.</li> </ol>	Each step - 1/2 M

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: 22330

	The current flowing through any element can be found out by substituting the value of node voltages in the relevant equation.	
e)	Write the formula for star to delta.	2M
Ans:	<p>The formula for star to delta</p> <p><b><u>Star to Delta (Y to Δ) Resistance Conversion Formula</u></b></p> $R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$ $R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$ $R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$	Correct formulae with diagram- 2M
f)	State Thevenin's theorem.	2M
Ans:	Any network containing active and/or passive elements and one or more dependent and/or independent voltage/or current sources can be replaced by an equivalent network containing a voltage source (Thevenin's equivalent voltage $V_{TH}$ or $V_{OC}$ ) and a series resistance (called Thevenin's equivalent resistance $R_{TH}$ ) where $V_{TH}$ is the voltage measured across open terminals A and B and $R_{th}$ is the resistance across same terminals A and B when all the sources are replaced by their internal resistances.	Statement (2 Mark)
g)	State the significance of two port network.	2M
Ans:	The significance of two port network-	2M

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network


Model Answer

Subject Code: 22330

Any electrical network can be easily analyzed if it is represented with an equivalent model, which gives the relation between input and output variables. A two port network is a network having 2 ports. One port is used as input port and the other port is used as output port. These ports are called port1 and port2 respectively.

Once a network is represented in this equivalent form, the response of the network to signals applied to the ports can be calculated easily, without solving for all the internal voltages and currents in the network. It also allows similar circuits or devices to be compared easily.

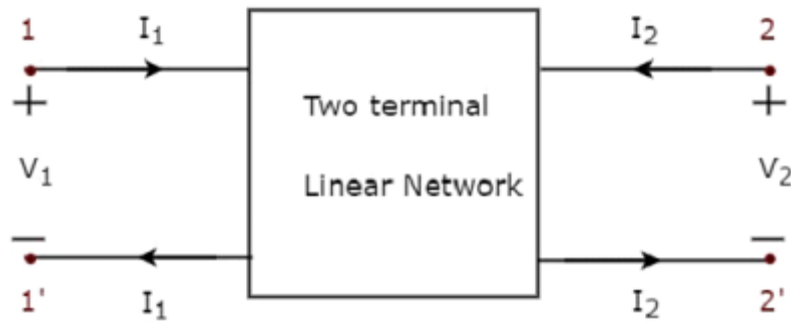A two port network representation is shown in the following figure.



Here, terminals 1 and 1' represent port1 and terminals 2 & 2' represent port2.

The common models that are used are referred to as z-parameters, y-parameters, h-parameters, g-parameters, and ABCD-parameters..

Q. No.	Sub Q. N.	Answers	Marking Scheme
2		<b>Attempt any THREE of the following:</b>	<b>12- Total Marks</b>
	a)	<b>An RC series circuit consists of <math>R = 10\Omega</math> and <math>C = 200 \mu\text{f}</math>.it is connected across 250 V, 50Hz, 1 <math>\phi</math> AC. Calculate the value of power consumed by the circuit.</b>	<b>4M</b>
	Ans:		1M - $X_c$ , 1M-Z,


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code **22330**

5

	<p>Solution -:</p> <p>Given -:</p> $R = 10\Omega, C = 200\mu F, V = 250V, f = 50\text{ Hz}$ <p>Capacitive Reactance, <math>X_C</math> :-</p> $X_C = \frac{1}{2\pi fC}$ $= \frac{1}{2 \times \pi \times 50 \times 200 \times 10^{-6}}$ $\therefore X_C = 15.91\Omega$ <p><math>\therefore</math> Impedance <math>Z</math> :-</p> $\therefore  Z  = \sqrt{R^2 + X_C^2} = \sqrt{10^2 + (15.91)^2}$ $\therefore  Z  = 18.79\Omega$ <p>Now, the total current <math>I</math> :</p> $\therefore I = \frac{V}{Z} = \frac{250}{18.79} = 13.30\text{ A}$ <p>Power Factor, <math>\cos \phi = \frac{R}{Z} = \frac{10}{18.79}</math></p> $\therefore \text{P.F.} = \cos \phi = 0.53 \text{ (leading)}$ <p>And, the value of Power consumed by the circuit is P:-</p> $P = V \cdot I \cos \phi$ $= 250 \times 13.30 \times 0.53$ $\therefore P = 1762.25 \text{ watt}$ <p>OR <math>\therefore P = 1.7622 \text{ Kwatt}</math></p> 	<p>1M- Power Factor,  1M- Power consumed</p>
<p>b)</p>	<p><b>Describe the procedure to tune the given electrical circuit using the principles of resonance.</b></p>	<p><b>4M</b></p>
<p>Ans:</p>	<p>An electrical circuit can be tuned to resonant frequency in any one of the following ways:</p>	<p><b>4M</b></p>


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: **22330**

6

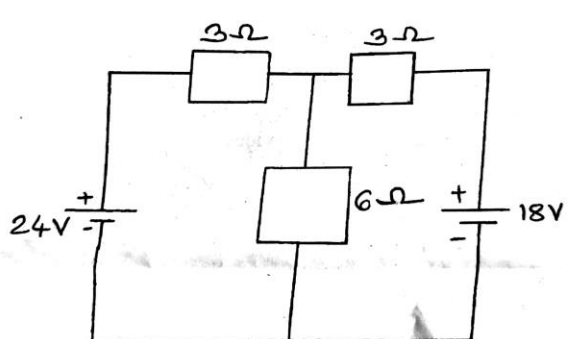	<p>i) If the circuit parameters like resistance, inductance and capacitance are of fixed value, the resonant frequency is calculated. Then by connecting a function generator, the input frequency can be varied till the circuit is tuned to the desired resonant frequency.</p> <p>ii) If the circuit is to be tuned to a particular frequency, and the frequency of the supply cannot be varied, then by using either a variable capacitor or variable inductor, the variable element can be varied till the circuit is tuned to the desired resonant frequency.</p>	
c)	<p>Find the current in <math>6\Omega</math> resistor in the circuit shown in Fig. No. 1 using mesh analysis.</p>  <p><u>Fig. No. 1</u></p>	4M



SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network


Model Answer

Subject Code 22330

7

Ans:

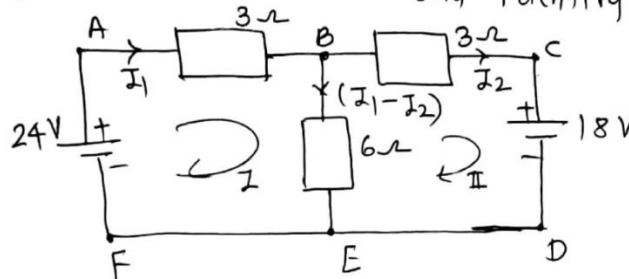Step 1 :- Name the nodes and identify the loops :-



Step 2 :- Equation for loop I (A B E F A) :-

Apply KVL,

$$\begin{aligned} 24 - 3I_1 - 6(I_1 - I_2) &= 0 \\ -3I_1 - 6I_1 + 6I_2 &= -24 \\ -9I_1 + 6I_2 &= -24 \\ \therefore 9I_1 - 6I_2 &= 24 \quad \text{--- (1)} \end{aligned}$$

Step 3 :- Equation for loop II (B C D E B) :-

$$\begin{aligned} -3I_2 - 18 - 6(I_2 - I_1) &= 0 \\ -3I_2 - 6I_2 + 6I_1 &= 18 \\ 6I_1 - 9I_2 &= 18 \quad \text{--- (2)} \end{aligned}$$

Solving equation (1) and (2) by Determinant Method

$$\begin{aligned} D &= \begin{vmatrix} 9 & -6 \\ 6 & -9 \end{vmatrix} = (-9) \times 9 - [(-6) \times 6] \\ &= -81 + 36 \\ \therefore D &= -45 \end{aligned}$$

$$\begin{aligned} D_1 &= \begin{vmatrix} 24 & -6 \\ 18 & -9 \end{vmatrix} = 24 \times (-9) - [(-6) \times 18] \\ &= -216 + 108 \\ \therefore D_1 &= -108 \end{aligned}$$

$$\begin{aligned} D_2 &= \begin{vmatrix} 9 & 24 \\ 6 & 18 \end{vmatrix} = 9 \times 18 - (24 \times 6) \\ &= 162 - 144 \\ \therefore D_2 &= 18 \end{aligned}$$

$$\therefore I_1 = \frac{D_1}{D} = \frac{-108}{-45} = 2.4 \text{ A}$$

$$I_2 = \frac{D_2}{D} = \frac{18}{-45} = -0.4 \text{ A}$$

$$\begin{aligned} \therefore \text{The current in } 6\Omega \text{ resistor is } (I_1 - I_2) \\ &= 2.4 - (-0.4) \\ &= 2.8 \text{ A} \end{aligned}$$

½ M-  
each  
equation

1M for  
I<sub>1</sub>,

1M for  
I<sub>2</sub>,

1M for  
current  
through  
6 ohm  
resistor



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

- d) Find the value of  $R_L$  so that maximum power will transfer from source to it . also write equation for  $P_{MAX}$  (Fig. No. 2)

4M

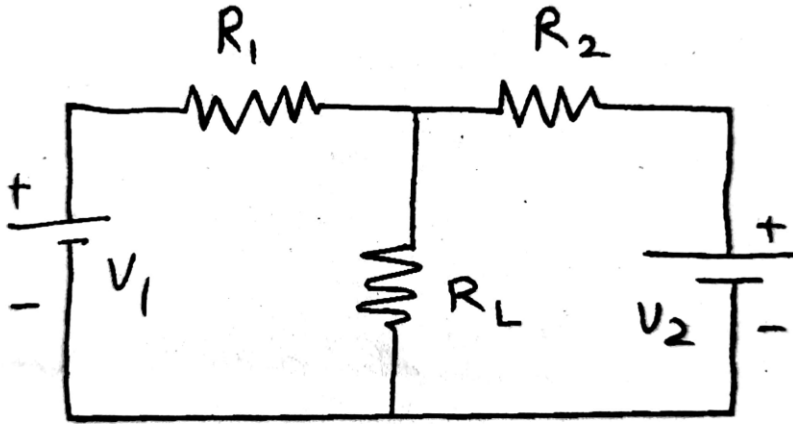


Fig. No. 2




SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330
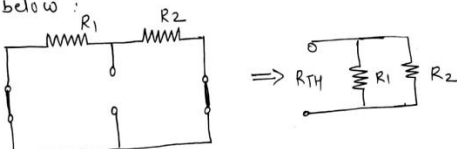
<p>Ans:</p>	<p>Replace the voltage sources <math>V_1</math> and <math>V_2</math> by short circuit to obtain the circuit shown below :</p>  <p><math>\therefore R_{TH} = R_1 \parallel R_2</math>  <math>\therefore R_{TH} = \frac{R_1 \times R_2}{R_1 + R_2}</math></p> <p>But the condition for maximum power transfer to the load is -  <math>R_L = R_{TH}</math>.</p> <p><math>\therefore</math> The value of <math>R_L = R_{TH}</math> so that maximum power will transfer from source to it.</p> <p>The equation for <math>P_{max}</math> -</p> $P_{L(max)} = \left( \frac{V_{TH}}{R_{TH} + R_{TH}} \right)^2 R_{TH}$ <p>Substitute <math>R_L = R_{TH}</math></p> <p><math>\therefore</math> Therefore the power transfer to the load is given by the equation</p> $P_L = \frac{V_{TH}^2}{4 R_{TH}}$	<p>3M-for <math>R_L</math> 1M for power formula</p>	
<p>Q. No.</p>	<p>Sub Q. N.</p>	<p>Answers</p>	<p>Marking Scheme</p>
<p>3</p>	<p>Attempt any THREE of the following :</p>		<p>12- Total Marks</p>
	<p>a)</p>	<p>List the power factor improves technique and explain any one with advantage and disadvantage</p>	<p>4M</p>
	<p>Ans:</p>	<p>Power factor improvement techniques are</p> <ul style="list-style-type: none"> <li>i) Synchronous Motors (or capacitors)</li> <li>ii) Static Capacitors</li> </ul>	<p>2Marks for Listing Techniques</p>





SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

10

		<p><b>iii) Phase Advancers</b></p> <p><b>i) Synchronous Motors (or capacitors) :</b> These machines draw leading kVAR when they are over-excited and, especially, when they are running idle. They are employed for correcting the power factor in bulk and have the special advantage that the amount of correction can be varied by changing their excitation.</p> <p><b>ii) Static Capacitors :</b> They are installed to improve the power factor of a group of a.c. motors and are practically loss-free (i.e. they draw a current leading in phase by 90°). Since their capacitance is not variable, they tend to over-compensate on light loads, unless arrangements for automatic switching of the capacitor bank are made.</p> <p><b>iii) Phase Advancers :</b> They are fitted with individual machines. However, it may be noted that the economical degree of correction to be applied in each case, depends upon the tariff arrangement between the consumers and the supply authorities.</p>	<p>2Marks for any one technique</p>																
	<b>b)</b>	<p>Compare series resonance to parallel resonance on the basis of:</p> <p>(i) Resonant frequency (ii) Impedance (iii) Current and (iv) Magnification.</p>	<p>4M</p>																
	<b>Ans:</b>	<table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 10%;">S.No.</th> <th style="width: 25%;">Parameter</th> <th style="width: 30%;">Series Circuit</th> <th style="width: 35%;">Parallel Circuit</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">1</td> <td>Resonant frequency</td> <td style="text-align: center;"><math>f_r = \frac{1}{2\pi\sqrt{LC}}</math></td> <td style="text-align: center;"><math>f_r = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}</math></td> </tr> <tr> <td style="text-align: center;">2</td> <td>Impedance</td> <td>Minimum, <math>Z = R</math></td> <td>Maximum, <math>Z = L/CR</math></td> </tr> <tr> <td style="text-align: center;">3</td> <td>Current</td> <td>Maximum, <math>I = V/R</math></td> <td>Minimum, <math>I = V/(L/CR)</math></td> </tr> </tbody> </table>	S.No.	Parameter	Series Circuit	Parallel Circuit	1	Resonant frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$	2	Impedance	Minimum, $Z = R$	Maximum, $Z = L/CR$	3	Current	Maximum, $I = V/R$	Minimum, $I = V/(L/CR)$	<p>1 marks for each point</p>
S.No.	Parameter	Series Circuit	Parallel Circuit																
1	Resonant frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$																
2	Impedance	Minimum, $Z = R$	Maximum, $Z = L/CR$																
3	Current	Maximum, $I = V/R$	Minimum, $I = V/(L/CR)$																

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

	4	Magnification	Voltage magnification takes place	Current magnification takes place	
c)		Write the procedure to convert voltage source into equivalent current source. Give its application. Draw neat diagrams of both the sources.			4M
Ans:		<p>A voltage source with a series resistance can be converted into (or replaced by) and equivalent current source with a parallel resistance.</p> <p>The steps for converting practical voltage source into practical current source.</p> <p>i) Find the value of current supplied by the source when a 'short' is put across terminals A and B.</p> <p>Therefore,</p> <p style="text-align: center;"><math>\text{Current } I = V/R</math></p> <p>ii) The value of resistance which is connected in parallel with the equivalent current source have the same value of series resistance (<math>R_s = R_{sh}</math>).</p> <p>ii) This equivalent current source is then connected in parallel with the shunt (parallel) resistance.</p> <div style="text-align: center; margin-top: 20px;"> </div>			2 marks for Procedure
					1 mark for diagram


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

12

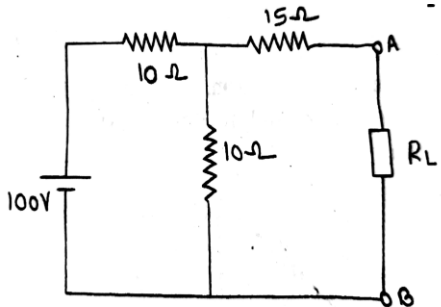	<p><b>Application :</b> For the simplification and analysis of complex networks the transformation of voltage source to an equivalent current source or vice versa is often necessary.</p>	<p><b>1 mark for Application</b></p>
<p><b>d)</b></p>	<p><b>Find Norton's equivalent circuit of the Fig. shown (Fig. No. 3)</b></p> <div style="text-align: center;"></div> <p><b>Fig. No. 3</b></p>	<p><b>4M</b></p>
<p><b>Ans:</b></p>		


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

13

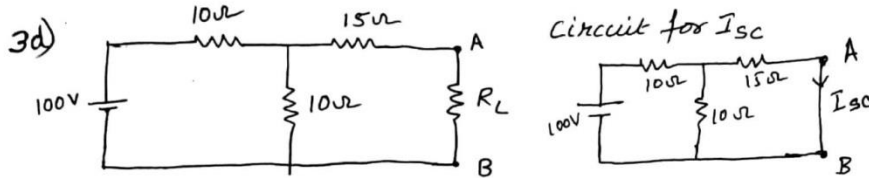

Step 1: To obtain the value of  $I_{sc}$ :

The Total resistance  $R_T$  is given by

$$R_T = 10 + [10 || 15]$$

$$= 10 + \left[ \frac{10 \times 15}{10 + 15} \right]$$

$$= 10 + 6 = 16 \Omega$$

The Source current  $I$  is given by


$$I = \frac{V}{R_T} = \frac{100}{16} = 6.25 \text{ A}$$

The short circuit current  $I_{sc}$  is the current flowing through the  $15 \Omega$  resistor

$$\therefore I_{sc} = I \times \frac{10}{10 + 15} = 6.25 \times \frac{10}{25}$$

$$I_{sc} = 2.5 \text{ A}$$


Step 2: To obtain the value of  $R_{th}$

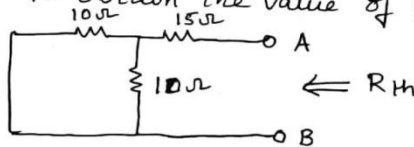

$$\therefore R_{th} = 15 + [10 || 10]$$

$$= 15 + 5 = 20 \Omega$$

Step 3: Norton's equivalent circuit

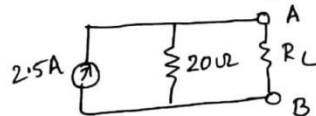

2marks for obtaining Short circuit current

1mark for  $R_{th}$

1mark for equivalent circuit



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

14

Q. No.	Sub Q. N.	Answers	Marking Scheme
4		Attempt any THREE of the following :	12- Total Marks
	(a)	<p>In a series circuit containing pure resistance pure inductance, the current and voltage are expressed as:</p> <p><math>I(t) = 5 \sin (314t + 2 \pi/3)</math> and <math>v(t) = 20 \sin (314t + 5 \pi/6)</math></p> <p>Find:</p> <ul style="list-style-type: none"> <li>(i) Impedance of circuit</li> <li>(ii) Resistance of circuit</li> <li>(iii) Inductance in circuit</li> <li>(iv) Average power drawn by circuit.</li> </ul>	4M
	Ans:	<p><math>I(t) = 5 \sin (314t + 2 \pi/3)</math> and <math>v(t) = 20 \sin (314t + 5 \pi/6)</math></p> <p>Converting the above standard sinusoidal forms into polar forms</p> <p>Rms values of current and voltage are</p> <p><math>I = 5/\sqrt{2} = 3.54 \text{ A}</math> ; <math>V = 20/\sqrt{2} = 14.14 \text{ V}</math></p> <p>Converting the above standard sinusoidal forms into polar forms</p> <p><math>\vec{I} = (3.54 \angle 120^\circ) \text{ A}</math></p> <p><math>\vec{V} = (14.14 \angle 150^\circ) \text{ V}</math></p> <p>By Ohm's law,</p> <p>Circuit Impedance, <math>\vec{Z} = \vec{V} / \vec{I} = (14.14 \angle 150^\circ) / (3.54 \angle 120^\circ)</math></p> <p style="text-align: center;"><math>= (4 \angle 30^\circ) \Omega</math></p>	1 mark for Impedance



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

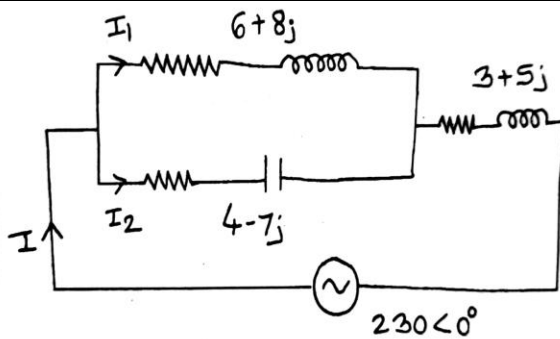


Fig. No. 4

Ans:


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

17

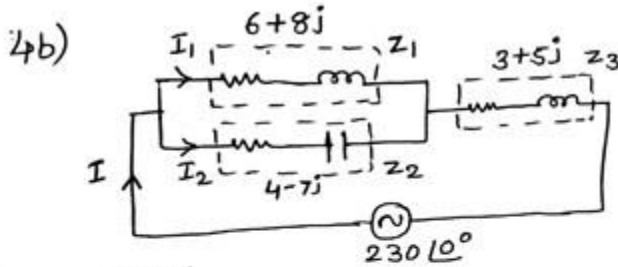

sol Given:  
 $Z_1 = 6 + 8j$ ,  $Z_2 = 4 - 7j$ ,  $Z_3 = 3 + 5j$ ,  $V = 230 \angle 0^\circ$

Total Impedance

$$Z = (Z_1 \parallel Z_2) + Z_3 = \frac{Z_1 Z_2}{Z_1 + Z_2} + Z_3$$

But  $Z_1 + Z_2 = 6 + 8j + 4 - 7j$   
 $= 10 + j$   
 $= 10 \angle 5.71^\circ$

Polar form of  $Z_1 = (10 \angle 53.13)$

" "  $Z_2 = (8.06 \angle -60.25)$

$$\therefore \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(10 \angle 53.13) \times (8.06 \angle -60.25)}{10 \angle 5.71}$$

$$= \frac{80.6 \angle -7.12}{10 \angle 5.71} = 8.06 \angle -12.83^\circ$$

$$= 7.85 - 1.78j$$

$$\therefore Z = 7.85 - 1.78j + 3 + 5j$$

$$= 10.85 + 3.22j$$

$$= 11.31 \angle 16.52^\circ$$

• Total current  $I = \frac{V}{Z} = \frac{230 \angle 0}{11.31 \angle 16.52}$

$$\therefore I = 20.33 \angle -16.52^\circ \text{ A}$$

•  $I_1 = I \times \frac{Z_2}{Z_1 + Z_2} = (20.33 \angle -16.52) \frac{8.06 \angle -60.25}{10 \angle 5.71}$

$$= (20.33 \angle -16.52) (0.806 \angle -65.96)$$

$$\underline{I_1 = 16.38 \angle -82.48^\circ \text{ A}}$$

1mark  
for I

1mark  
for I<sub>1</sub>

1mark  
for I<sub>2</sub>

1mark  
for  
Power  
factor



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

$$\begin{aligned}
 \bullet I_2 &= I \times \frac{Z_1}{Z_1 + Z_2} = (20.33 \angle -16.52) \frac{(10 \angle 53.13)}{(10 \angle 5.71)} \\
 &= (20.33 \angle -16.52) (1 \angle 47.42) \\
 \therefore I_2 &= \underline{20.33 \angle 30.9^\circ \text{ A}} \\
 \bullet \text{ power factor} &= \cos \phi = \cos (-16.52) \\
 &= \underline{0.958 \text{ lagging}}
 \end{aligned}$$


(c) Explain the term bandwidth of a series resonant circuit. Derive its equation.

4M

Ans: Band width (BW) of a series resonance circuit is defined as the range of frequency over which circuit current is equal to or greater than  $\frac{I_r}{\sqrt{2}}$  or 70.7 % of maximum current where  $I_0$  or  $I_r$  = current at resonance.

Explanation 2 Marks

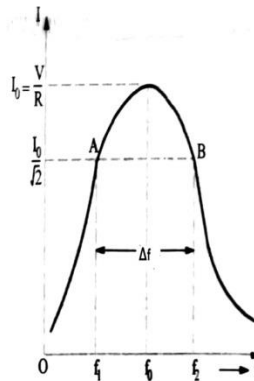The resonance curve for a series RLC circuit is shown below:



From the graph it is clear that for all frequencies lying between  $f_1$  and  $f_2$  the circuit current is equal to or greater than 70.7 % of maximum current i.e.



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code **22330**

19

$$I_r = V/R$$

Thus Band width of the circuit,  $BW = \Delta f = (f_2 - f_1)$  Hz

$$\text{Or } BW = \Delta \omega = (\omega_2 - \omega_1) \text{ rad/sec}$$

Derivation of equation for bandwidth -

The relationship between bandwidth , Q factor and resonant frequency is given by

$$(f_2 - f_1) = f_r / Q_r$$

Where  $f_2 - f_1 =$  bandwidth,  $f_r =$  resonant frequency and  $Q_r =$  Q factor at resonance

$$\text{But } f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$\text{And } Q_r = \frac{1}{R} \sqrt{\frac{L}{C}}$$

Substituting these values in the equation for bandwidth,

$$\Delta f = f_r / Q_r = \frac{\frac{1}{2\pi\sqrt{LC}}}{\frac{1}{R}\sqrt{\frac{L}{C}}} = \frac{R\sqrt{C}}{2\pi\sqrt{CL^2}} = \frac{R}{2\pi L} \text{ Hz}$$

$$\text{Therefore bandwidth } \Delta f = f_2 - f_1 = \frac{R}{2\pi L} \text{ Hz}$$

OR

$$\Delta \omega = 2\pi \Delta f = \frac{R}{L} \text{ rad/sec}$$

2marks  
for  
Derivati  
on


SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

20

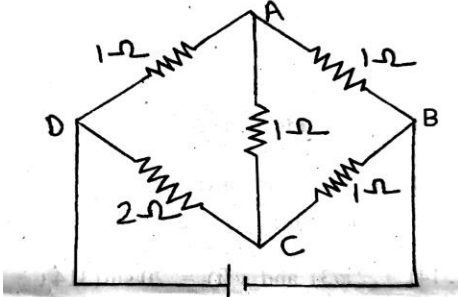
<p>(d)</p>	<p>A bridge network ABCD has arms AB, BC, CD and DA of resistances 1, 1, 2 and 1 ohm respectively . If the detector AC has a resistance of 1 ohm, determine by star/delta transformation, the network resistance as viewed from the battery terminals.</p> <div style="text-align: center;">  <p>Fig. No. 5</p> </div>	<p>4M</p>
<p>Ans:</p>		<p>2 marks for Converting delta to star</p> <p>2 marks for Network resistance</p>

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

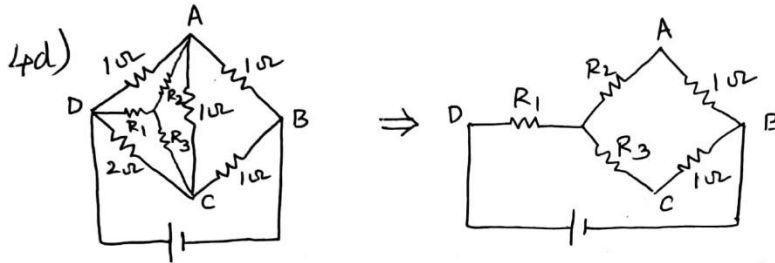


Step 1: Converting the delta formed by ACD into equivalent star network.

(ie)  $\Delta ACD \Rightarrow Y ACD$


$$\therefore R_1 = \frac{1 \times 2}{1+2+1} = \frac{2}{4} = 0.5 \Omega$$

$$R_2 = \frac{1 \times 1}{1+2+1} = \frac{1}{4} = 0.25 \Omega$$

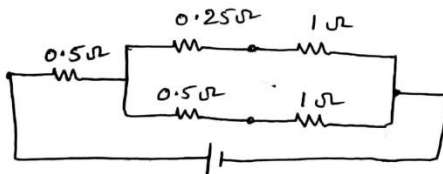
$$R_3 = \frac{1 \times 2}{1+2+1} = \frac{2}{4} = 0.5 \Omega$$



The above circuit is converted as

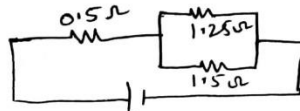

Here  $1.25 \Omega$  &  $1.5 \Omega$  are in parallel  
 $[1.25 || 1.5] = 0.68$

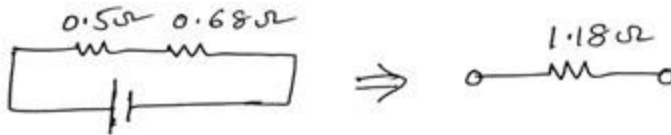

$\therefore$  network resistance = 1.18  $\Omega$

Note: The problem can be done by converting delta ABC into equivalent star also.

(e) Find current through  $6 \Omega$  resistor using superposition theorem. Fig. No. 6

4M



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code **22330**

22

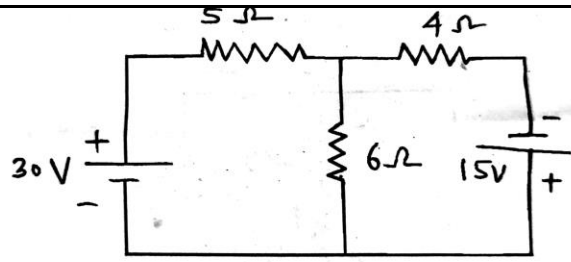


Fig. No. 6

Ans:

1mark  
for R<sub>T</sub>

SUMMER-19 EXAMINATION


Subject Name: Electric circuits and network

Model Answer

Subject Code 22330


23

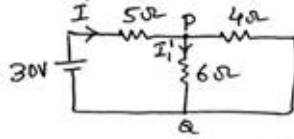4e) Replace the 15V source by a short circuit, keeping 30V



Resistor 6Ω & 4Ω are parallel  
 $\therefore 6 \parallel 4 = 2.4\Omega$

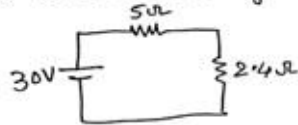→ Current through 6Ω Resistor due to 30V source is  $I_1$



Resistor 5Ω & 2.4Ω are in series

Total Resistance


$$R_T = 5 + 2.4 = 7.4\Omega$$

$$R_T = 7.4\Omega$$

$$\therefore \text{Total current } I = \frac{30}{7.4} = 4.05\text{A}$$


$$\therefore I_1 = I \times \frac{4}{4+6} = 4.05 \times \frac{4}{10} = \underline{1.62\text{A}}$$

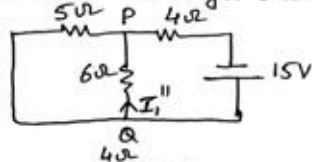→ Current through 6Ω Resistor due to 15V source is  $I_1''$



Resistor 5Ω & 6Ω are in parallel

$$\therefore 5 \parallel 6 = \frac{30}{11} = 2.72\Omega$$

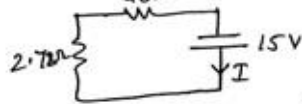

Resistor 2.72Ω & 4Ω are in series

$\therefore$  Total Resistance is

$$R_T = 2.72 + 4 = 6.72\Omega$$

$$\therefore \text{Total current } I = \frac{V}{R_T} = \frac{15}{6.72} = 2.23\text{A}$$

$$\therefore I_1'' = I \times \frac{5}{5+6} = 2.23 \times \frac{5}{11}$$

$$I_1'' = -1.01\text{A} \quad (\text{As current is flowing from Q to P we will consider it to be negative})$$

$\therefore$  Total current in 6Ω Resistor is (from P to Q)

$$I_1' + I_1''$$

$$= 1.62 - 1.01$$

$$I_{6\Omega} = 0.61\text{A}$$

1mark  
for  $I_1'$

1mark  
for  $I_1''$

1mark  
for  $I_{6\Omega}$



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: **22330**

24

Q. No.	Sub Q. N.	Answers	Marking Scheme
5.		<b>Attempt any TWO of the following:</b>	<b>12- Total Marks</b>
	a)	<b>A coil of resistance <math>20 \Omega</math> and <math>200 \mu\text{H}</math> is in parallel with a variable capacitor. The voltage of the supply is <math>20 \text{ V}</math> at a frequency of <math>10^6 \text{ Hz}</math>. Calculate :</b>  <b>(i) The value of C to give resonance.</b> <b>(ii) The Q of the coil.</b> <b>(iii) The current in each branch of the circuit at resonance.</b>	<b>6M</b>

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

Ans:

Q. 59) Diagram  $\Rightarrow$

Pg. No. ①

Dia 1 M

i) The value of 'c' to give resonance

\* If value of 'R' is considered very small in comparison with inductor 'L' then

$$\therefore f_r = \frac{1}{2\pi\sqrt{LC}} \quad \Rightarrow \quad \frac{1}{2} \text{ M}$$

$$\therefore (10^6) = \frac{1}{2\pi\sqrt{200 \times 10^6 \times C}}$$

Squaring to both sides.

$$(10^6)^2 = \frac{1}{4\pi^2 \times 200 \times 10^6 \times C}$$

$$\therefore C = \frac{1}{(10^6)^2 \times 4\pi^2 \times 200 \times 10^6}$$

OR

$$C = \frac{1}{126.65 \times 10^{10}} \text{ F} \quad \Rightarrow \quad \frac{1}{2} \text{ M}$$

\* If value of 'R' is considered very high in comparison with inductor 'L' then

$$\therefore f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad \Rightarrow \quad \frac{1}{2} \text{ M}$$

Squaring to both sides

$$\therefore f_r^2 = \frac{1}{4\pi^2} \left[ \frac{1}{LC} - \frac{R^2}{L^2} \right]$$

$$\therefore f_r^2 * 4\pi^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

$$f_r^2 * 4\pi^2 + \frac{R^2}{L^2} = \frac{1}{LC}$$

$$(10^6)^2 * 4\pi^2 + \frac{(20)^2}{(200 \times 10^6)^2} = \frac{1}{LC}$$



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

$$3.948 \times 10^{15} = \frac{1}{LC}$$

$$3.948 \times 10^{15} \times 200 \times 10^{-6} = \frac{1}{C}$$

$$C = 126.65 \text{ PF} \Rightarrow \text{1/2 M}$$

ii) The Q of the coil  

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$

$$= \frac{1}{20} \sqrt{\frac{200 \times 10^{-6}}{126.65 \times 10^{-12}}}$$

$$Q = 62.832 \Rightarrow \text{1 M}$$

OR  

$$Q = \frac{X_L}{R} = \frac{2\pi f L}{R} = \frac{2\pi \times 10^6 \times 200 \times 10^{-6}}{20}$$

$$Q = 62.832 \Rightarrow \text{1 M}$$

iii) The current in each branch of the circuit at resonance  
 Since this is a parallel circuit. We presume the applied voltage will be across each reactive element.  

$$i) X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 10^6 \times 126.65 \times 10^{-12}} = 1.256 \text{ k}\Omega$$

$$ii) X_L = 2\pi f L = 2\pi \times 10^6 \times 200 \times 10^{-6} = 1.256 \text{ k}\Omega \Rightarrow \text{1 M}$$

$$I_C = \frac{V}{X_C} = \frac{20}{1.256 \times 10^3} = 15.92 \text{ mA} \Rightarrow \text{1 M}$$

$$I_L = \frac{V}{X_L} = \frac{20}{1.256 \times 10^3} = 15.92 \text{ mA} \Rightarrow \text{1 M}$$

b) Find current through impedance  $3 + j5$  using superposition theorem in the circuit as shown in Fig. No. 7.

6M



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: 22330

27

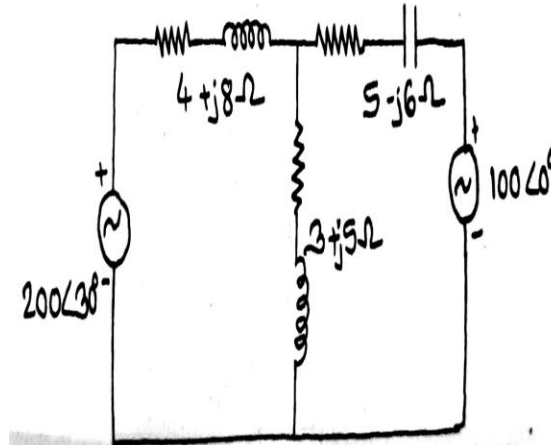


Fig. No. 7

SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

Ans:

Q.5 b)

Step 1: - convert  $V_1$  &  $V_2$  into rectangular form

$$V_1 = 200 \angle 30^\circ = 173.21 + j100$$

$$V_2 = 100 \angle 0^\circ = 100 + j0$$

find the current thr<sup>ough</sup> Branch 'AB' as  $I_1$  due to source  $V_1 = 200 \angle 30^\circ$

$\Rightarrow$  2 Marks

The impedances  $(5-j6)\Omega$  and  $(3+j5)\Omega$  are in parallel and this combination is in series with  $(4+j8)\Omega$

$$R_{Th} = \frac{(5-j6) * (3+j5)}{(5-j6) + (3+j5)} = \frac{15 + j25 - j8 + 30}{8-j1}$$

$$= \frac{45 + j7}{8-j1} = \frac{45.54 \angle 8.84^\circ}{8.062 \angle -7.13^\circ}$$

$$R_{Th} = 5.65 \angle 15.97^\circ$$

$$I_1 = \frac{200 \angle 30^\circ}{5.65 \angle 15.97^\circ}$$

$$\therefore I_1 = 35.398 \angle -14.03^\circ$$

$$I_1' = \frac{(5-j6)}{(5-j5) + (3+j5)} * I_1 = \frac{5-j6}{8-j1} * 35.398 \angle -14.03^\circ$$

$$= \frac{7.810 \angle -50.19^\circ}{8.062 \angle -7.13^\circ} * 35.398 \angle -14.03^\circ$$

$$I_1' = 34.28 \angle -57.09^\circ$$

Scanned by CamScanner




SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

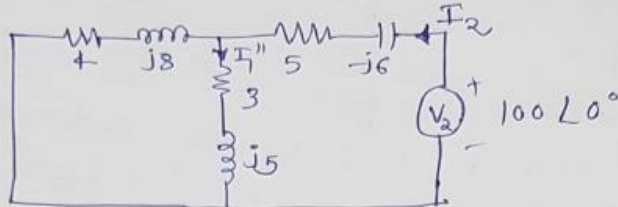Step 2 :- Similarly find current thr AB Branch  
Due to source  $V_2 = 100 \angle 0^\circ$



The impedances  $(4+j8)\Omega$  &  $(3+j5)\Omega$  are in parallel & this combination is in series with  $(5-j6)\Omega$

$$R_{th} = \frac{(4+j8)(3+j5)}{(4+j8)(3+j5)} = \frac{12+j20+j24-40}{(7+j13)}$$

$$= \frac{-28+j44}{7+j13} = \frac{52.15 \angle 122.47^\circ}{14.765 \angle 61.69^\circ}$$

$$\therefore R_{th} = 3.532 \angle 60.78^\circ$$

$$I_2 = \frac{100 \angle 0^\circ}{3.532 \angle 60.78^\circ}$$

⇒ 2 Marks

$$I_2 = 28.32 \angle -60.78^\circ$$

$$I_1'' = \frac{(4+j8)}{(7+j13)} * I_2$$

$$= \frac{(4+j8)}{(7+j13)} * 28.32 \angle -60.78^\circ$$

$$= \frac{8.944 \angle 63.43^\circ}{14.765 \angle 61.69^\circ} * 28.32 \angle -60.78^\circ$$

$$= \frac{8.944 * 28.32 \angle 63.43^\circ + (-60.78^\circ)}{14.765 \angle 61.69^\circ}$$

$$I_1'' = \frac{253.29 \angle 2.65^\circ}{14.765 \angle 61.69^\circ}$$

$$I_1'' = 17.15 \angle -59.04^\circ$$

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

Step 3:- current flowing thr<sup>h</sup> AB branch due to

$V_1$  is  $I_1' = 34.28 \angle -57.09$

$V_2$  is  $I_1'' = 17.15 \angle -59.04$

convert these currents into Rectangular form

$I_1' = 18.63 - j28.78$

$I_1'' = 8.823 - j14.71$

$\therefore I_{AB \text{ Branch}} = I_1' + I_1''$

$\therefore I_{AB \text{ Branch}} = I_1' + I_1''$  or c/n thr<sup>h</sup>  $(3+j5)$  Branch

$= 27.453 - j43.49$

$\therefore I_{AB \text{ Branch}} \stackrel{m}{=} I_{(3+j5)} = 51.48 \angle 57.74$

Pg No 03

2 Marks

c) Sketch the phasor diagram for the nominal drawn circuit with justification of each phasor drawn.

6M

Ans: Consider series R-L circuit

Phasor diagram of RL circuit

Where  $V_R$  = Voltage across the resistor 'R'

$V_L$  = Voltage across the inductor 'L'

$V$  = Total Voltage of the circuit

Circuit diagram : 1 Mark

Phasor diagram : 3 Marks



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: 22330

31

Explanation :-

In RL circuit Resistor 'R' & Inductor 'L' are connected in series with a voltage supply of  $V_s$ . Since both R & L are connected in series, so the current in both the elements of the circuit remains same.

$$\text{i.e. } I_R = I_L = I$$

Let  $V_R$  &  $V_L$  be voltage drop across resistor & inductor.

In Resistor, the voltage  $V_R$  &  $I_R$  are in phase. Whereas in inductor, the voltage  $V_L$  & current are not in phase. The voltage leads the current by  $90^\circ$ .

Explanation  
:2Marks


**Note:** If the student has attempted to solve the question considering any one of the following circuits : Series R-C or R-L-C circuit or Parallel R-L or R-C or R-L-C circuit, give appropriate marks.

SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

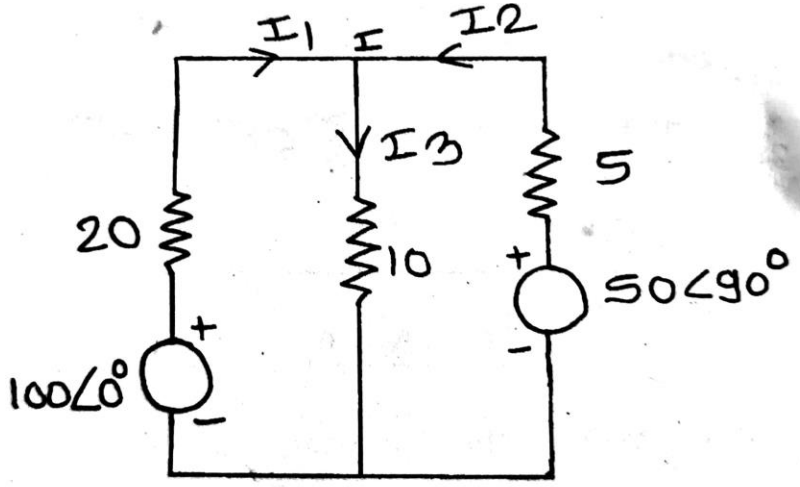Q. No.	Sub Q. N.	Answers	Marking Scheme
6.		Attempt any TWO of the following :	12- Total Marks
	a)	<p>Use nodal analysis to calculate the current flowing in each branch of the network shown in Fig. No. 8</p>  <p style="text-align: center;"><u>Fig. No. 8</u></p>	6M

SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: 22330

33

Ans:

Q.6 a) Using Nodal Analysis:

$100 \angle 0^\circ$   
 $\Rightarrow 100 + j0$

$50 \angle 90^\circ \Rightarrow (0 + j50)$

Applying Nodal analysis to node 'A'

$$\frac{100 - V_A}{20} - \frac{V_A}{10} + \frac{j50 - V_A}{5} = 0 \quad \Rightarrow \underline{\underline{1M}}$$

$$\frac{100 - V_A - 2V_A + j200 - 4V_A}{20} = 0$$

$$100 - 7V_A + j200 = 0$$

$$100 + j200 = 7V_A$$



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

$\frac{100 + j200}{7} = V_A$

$\therefore V_A = 31.94 \angle 63.43^\circ \text{ V} \implies \text{1M}$

$\therefore V_A = 14.29 + j28.566$

(a) current flowing thr  $20\Omega$  resistor

$I_{20\Omega} = \frac{(100 \angle 0^\circ) - (31.94 \angle 63.43^\circ)}{20}$

$= \frac{100 + j0 - 14.29 - j28.57}{20}$

$= \frac{100 - 14.29 - j28.57}{20} = \frac{85.72 - j28.56}{20}$

$= \frac{90.35 \angle -18.42^\circ}{20} \implies \text{2M}$

$I_{20\Omega} = 4.517 \angle -18.42^\circ \text{ Amp.}$   
or  $4.285 - j1.427 \text{ Amp.}$

(b) current flowing thr  $10\Omega$  resistor

$I_{10\Omega} = \frac{V_A}{10} = \frac{31.94 \angle 63.43^\circ}{10}$

$\therefore I_{10\Omega} = 3.194 \angle 63.43^\circ \text{ Amp.} \implies \text{1M}$

(c) current flowing thr  $5\Omega$  resistor

$I_{5\Omega} = \frac{j50 - 14.29 - j28.57}{5}$

$= \frac{-14.29 + j21.43}{5}$

$= \frac{25.757 \angle 123.69^\circ}{5}$

$I_{5\Omega} = 5.151 \angle 123.69^\circ \text{ Amp.} \implies \text{1M}$

b) Verify the reciprocity theorem in the circuit given in Fig. No. 9

6M



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code: 22330

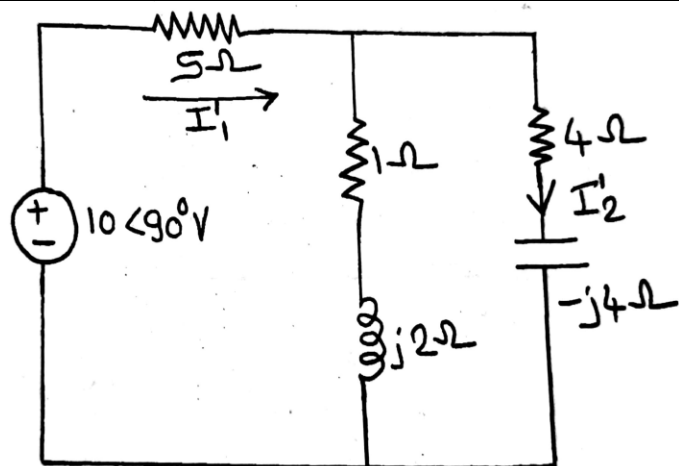


Fig. No. 9

Ans:


SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

Q6 b)

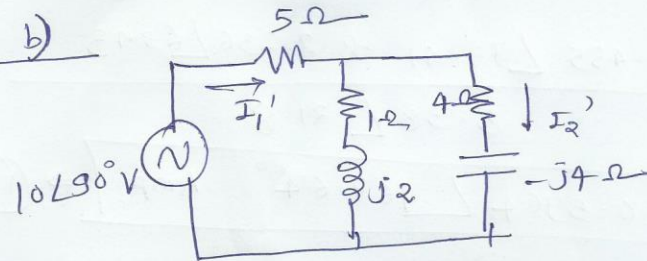

Case: 1  
Step 1: consider the given circuit as it is

$$\begin{aligned}
 Z_{eq} &= 5 + [(1 + j2)] \parallel [(4 - j4)] \\
 &= 5 + \frac{(1 + j2)(4 - j4)}{1 + j2 + 4 - j4} \\
 &= 5 + \frac{(4 - j4 + j8 + 8)}{5 - j2} \\
 &= 5 + \frac{12 + j4}{5 - j2} \\
 &= \frac{25 - j10 + 12 + j4}{(5 - j2)} \\
 &= \frac{37 - j6}{5 - j2} = \frac{37.48 \angle -9.21}{5.38 \angle -21.8}
 \end{aligned}$$

$$Z_{eq} = 6.966 \angle 12.59 \Omega \rightarrow (1M)$$

$$I_1' = \frac{10 \angle 90^\circ}{6.966 \angle 12.59} = 1.435 \angle +77.41 \text{ Amp.} \rightarrow (1M)$$

using c/n division rule,

$$\begin{aligned}
 I_2' &= 1.435 \angle 77.41 * \frac{(1 + j2)}{1 + j2 + 4 - j4} \\
 &= \frac{1.435 \angle 77.41 * (1 + j2)}{5 - j2}
 \end{aligned}$$

SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network


Model Answer

Subject Code 22330

$$= \frac{1.435 \angle 77.41^\circ \times 2.236 \angle 63.43^\circ}{5.38 \angle -21.8^\circ}$$

$$I_2' = 0.5964 \angle 162.64^\circ \text{ Amp} \Rightarrow (1M)$$

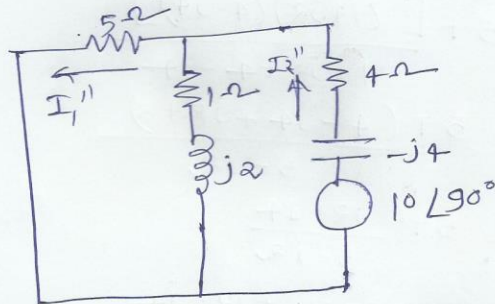Case 2: Change the position of voltage source  
Step 1:- calculate currents.



$$Z_{eq}' = \frac{5 + j10}{6 + j2} + (4 - j4)$$

$$= \frac{11.18 \angle 63.43^\circ}{6.32 \angle 18.43^\circ} + (4 - j4)$$

$$= (1.718 \angle 45^\circ) + (4 - j4)$$

$$= 1.25 + j1.25 + 4 - j4$$

$$= 5.25 - j2.75$$

$$Z_{eq}' = 5.926 \angle -27.64^\circ \Rightarrow (1M)$$

SUMMER-19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code 22330

38

$$I_2'' = \frac{10 \angle 90^\circ}{5.926 \angle -27.61}$$

$$I_2'' = 1.687 \angle 117.64 \text{ Amp}$$

using current division rule,

$$I_1'' = 1.687 \angle 117.64 * \frac{(1+j2)}{6+j2}$$

$$= \frac{1.687 \angle 117.64 * (2.236 \angle 63.43)}{6.32 \angle 18.43}$$

$$I_1'' = 0.596 \angle 162.64 \text{ Amp} \Rightarrow (1M)$$

Proof :- per Reciprocity th<sup>m</sup> statement,  
As case: 1 Ratio of voltage source to response is

$$\frac{V}{I_2'} = \frac{10 \angle 90^\circ}{0.596 \angle 162.64}$$

$$= 16.77 \angle -76.64 \Rightarrow (1M)$$

Case: 2  $\frac{V_1}{I_1''} = \frac{10 \angle 90^\circ}{0.596 \angle 162.64}$

$$= 16.77 \angle -76.64$$

As the transfer ratio is same in both cases.  
Thus the Reciprocity th<sup>m</sup> is verified.



SUMMER- 19 EXAMINATION

Subject Name: Electric circuits and network

Model Answer

Subject Code **22330**

c)	<p>Draw the two port network and determine the indicated parameters for the following configurations:</p> <ul style="list-style-type: none"><li>(i) Cascade configurations (ABCD parameter)</li><li>(ii) Series configurations</li><li>(iii) Parallel configurations.</li></ul>	6M

SUMMER- 19 EXAMINATION


Subject Name: Electric circuits and network

Model Answer


Subject Code 22330

Ans:

Cascade configuration ABCD parameter :-

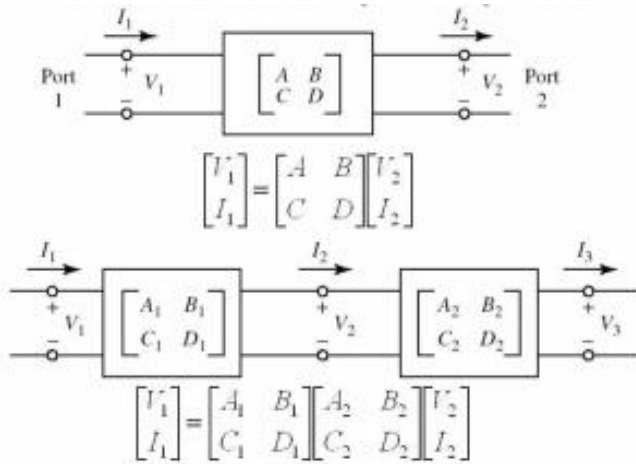


OR

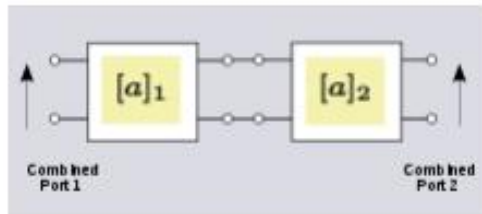


1 mark for the diagram and 1 mark for equation for each configuration

Series configurations:-

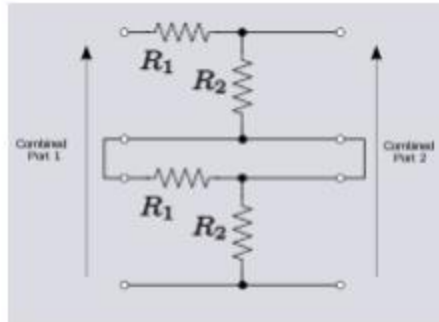

OR

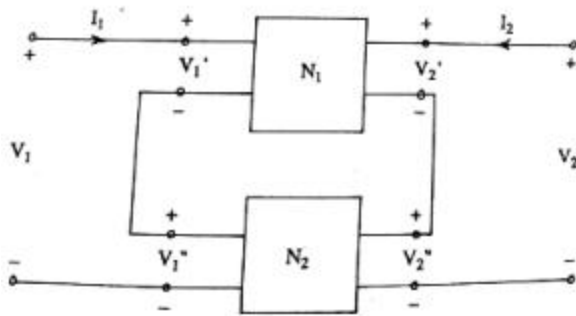

Where N1 and N2 are two port Network

$$[Z] = [Z_1] + [Z_2]$$


The Z parameter equation can be written as below

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

where  $Z_{11}$ ,  $Z_{12}$ ,  $Z_{21}$  and  $Z_{22}$  are sum of corresponding values of individual networks.



Parallel configurations:-

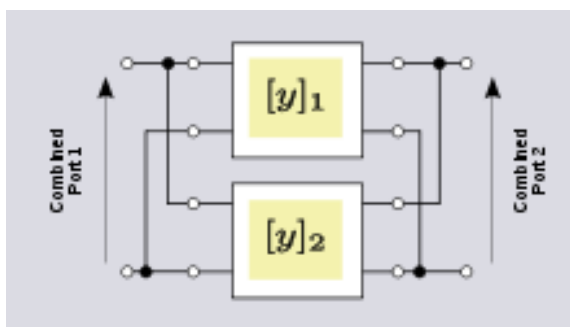

When two-ports are connected in a parallel configuration as shown in figure, The choice of two-port parameter is the y-parameters. The y-parameters of the combined network are found by matrix addition of the two individual y-parameter matrices.

$$[\mathbf{y}] = [\mathbf{y}]_1 + [\mathbf{y}]_2$$

Where Y parameter equation can be written as below

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

where  $Y_{11}$ ,  $Y_{12}$ ,  $Y_{21}$  and  $Y_{22}$  are sum of corresponding values of individual networks.



# V2V EDTECH LLP

Online Coaching at an Affordable Price.

## OUR COURSES:

- Diploma in All Branches, All Subjects
- Degree in All Branches, All Subjects
- BSCIT / CS
- Professional Courses



**+91 93260 50669**



**[www.v2vclass.com](http://www.v2vclass.com)**



**V2V EdTech LLP**



**v2vedtech**



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

1

**Important Instructions to examiners:**

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance (Not applicable for subject English and Communication Skills).
- 4) While assessing figures, examiner may give credit for principal components indicated in the figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case of some questions credit may be given by judgement on part of examiner of relevant answer based on candidate's understanding.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q. No.	Sub Q. N.	Answers	Marking Scheme
1	(A)	<b>Attempt any FIVE of the following:</b>	<b>10- Total Marks</b>
	(a)	<b>Define:</b>  (i) <b>Apparent power</b> (ii) <b>Real power</b>	<b>2M</b>
	<b>Ans:</b>	<b>(i) Apparent power</b> It is the product of rms values of applied voltage and circuit current. Unit: volt-ampere (VA) OR kilo-volt-ampere (kVA) OR Mega-volt-ampere (MVA) $S = VI = I^2 Z$ volt-ampere (VA) <b>(ii) Real power</b> The active power is defined as the average power $P_{avg}$ taken by or consumed by the given circuit.  <b>(OR)</b>	<b>1 M for each definition</b>



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

2

	It is the power which is actually dissipated in the circuit resistance. $P = V.I.\cos\phi$ Unit: - Watt OR Kilowatt	
<b>(b)</b>	<b>Write equation of resultant impedance in R-L circuit.</b>	<b>2M</b>
<b>Ans:</b>	<b>The equation of resultant impedance in R-L circuit</b> $Z = \sqrt{R^2 + X_L^2}$ Where ,R=Resistance $X_L = \text{Inductive Reactance} = 2\pi fL \Omega.$	<b>2 M for equation</b>
<b>(c)</b>	<b>State condition for resonance in R-L-C series circuit.</b>	<b>2M</b>
<b>Ans:</b>	<b>The condition for resonance in R-L-C series circuit.</b> i) Inductive Reactance should be equal to capacitive reactance. That is $X_L = X_C$ ii) The power factor of the circuit is $\cos \phi = 1$ iii) The voltage and current in the R-L-C series circuit are in phase with each other. iv) Current in the circuit is maximum and given by $I = V/R.$ v) Impedance of the circuit is minimum and given by $Z = R.$	<b>2M for any two conditions</b>
<b>(d)</b>	<b>Draw –</b> <b>(i) Practical voltage source</b> <b>(ii) Ideal current source</b>	<b>2M</b>
<b>Ans:</b>	<b>i) Practical voltage source</b>	<b>1 M for each diagram</b>


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network


Subject Code: 22330

Model Answer

3

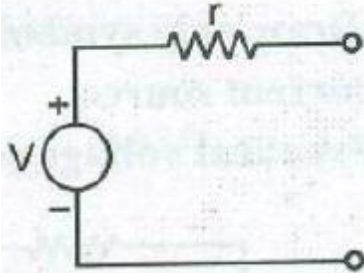

ii) Ideal current source

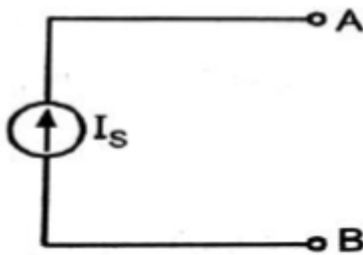


Where,  
 $I_s$  = Current Source  
 $R_s$  = internal resistance of source

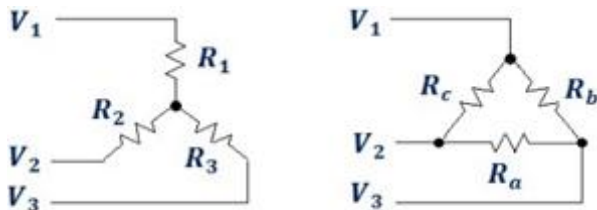e) Write formula for star to delta and delta to star transformation.

2M

Ans: The formula star to delta conversion



$$R_a = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_1 R_3 + R_2 R_3}{R_3}$$

1 M for  
star to  
delta  
transfor  
mation

1 M for  
delta to  
star  
transfor  
mation

WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

4

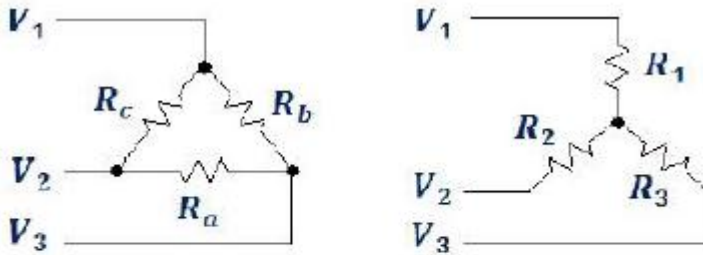The formula for Delta to Star conversion-



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

f) State maximum power transfer theorem.

2M

Ans: Maximum Power Transfer Theorem states that "Maximum power is transferred from the source to the load when the load resistance is equal to the Thevenin's equivalent resistance of the given circuit as seen from load terminals"  
.i. e,  $R_L = R_{TH}$

2M for statement

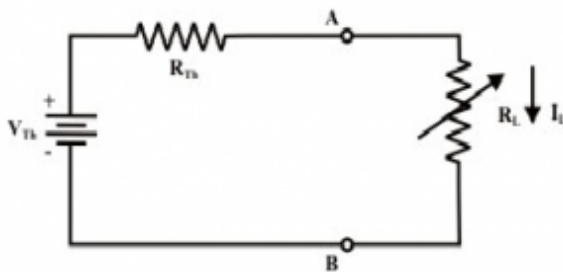

g) Write equation of short circuit Y parameters.

2M

Ans: The equation of short circuit Y parameters.

1 M for each equation



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330


Model Answer

5

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \dots\dots\dots 1$$
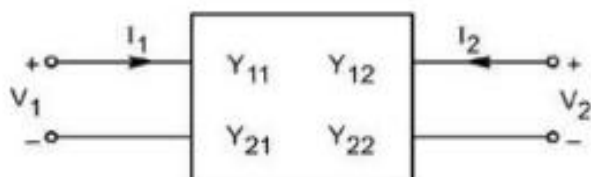
$$I_2 = Y_{21} V_1 + Y_{22} V_2 \dots\dots\dots 2$$



Q. No.	Sub Q. N.	Answers	Marking Scheme
2		Attempt any THREE of the following:	12- Total Marks
	a)	For R-C series circuit draw  (i) Circuit diagram (ii) Vector diagram (iii) Waveform of voltage and current	4M
	Ans:	i)Circuit diagram	1M- circuit diagram, 1M- vector diagram, 2M- wavefor ms


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network


Subject Code:

22330

Model Answer

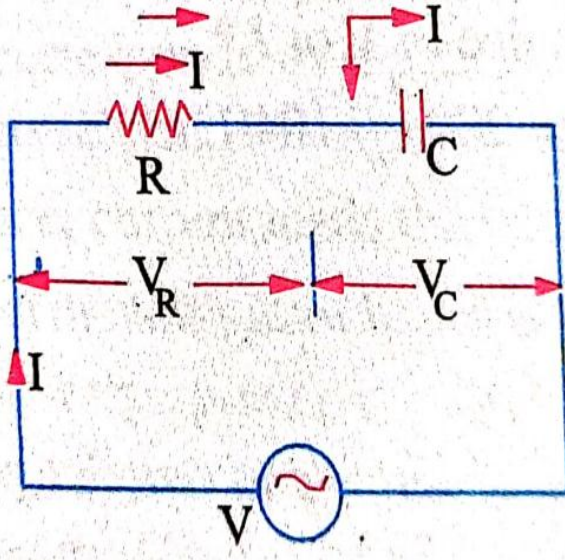

ii) Vector diagram

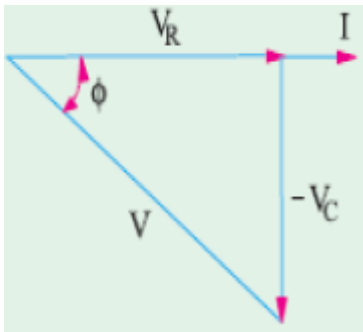

iii) Waveform of voltage and current




WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

7

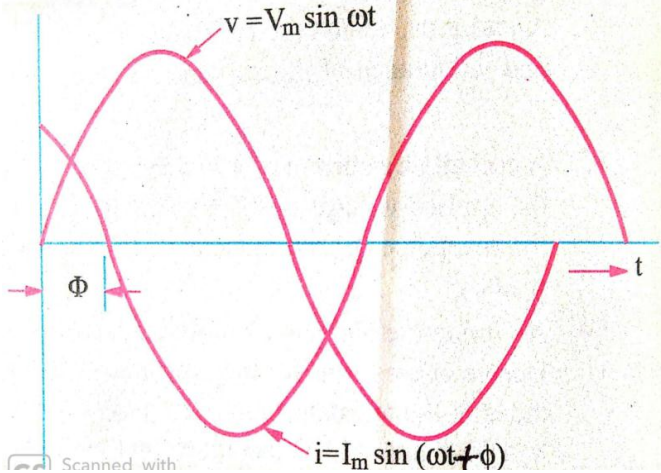

b) Compare series and parallel resonance on the basis of

- (i) Resonating frequency
- (ii) Impedance
- (iii) Current
- (iv) Magnification

4M

Ans:

S. No	Parameter	Series Circuit	Parallel Circuit
1	Resonating frequency	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$f_r = \frac{1}{2\pi\sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}}$
2	Impedance	Minimum, $Z = R$	Maximum, $Z = L/CR$
3	Current	Maximum, $I = V/R$	Minimum, $I = V/(L/CR)$
4	Magnification	Voltage magnification takes place	Current magnification takes place

1M for each point

c) Explain the suitable example to convert a practical current source into equivalent voltage source.

4M


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

Ans:

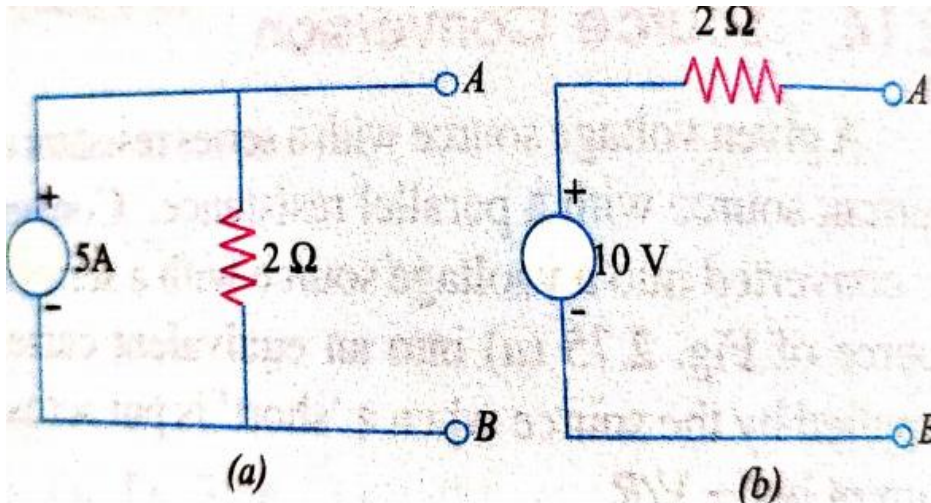

The open-circuit voltage across terminals A and B is

$$V_{oc} = \text{drop across } R \\ = 5 \times 2 = 10V$$

Hence, voltage source has a voltage of 10V and the same resistance of 2Ω

2M-  
circuit  
diagram,  
2M-  
conversi  
on

d) Write the steps for finding the current through an element by Thevenin's theorem.

4M

Ans: Steps to find Thevenin's equivalent circuit, taking an example is as follows:

1M each  
step

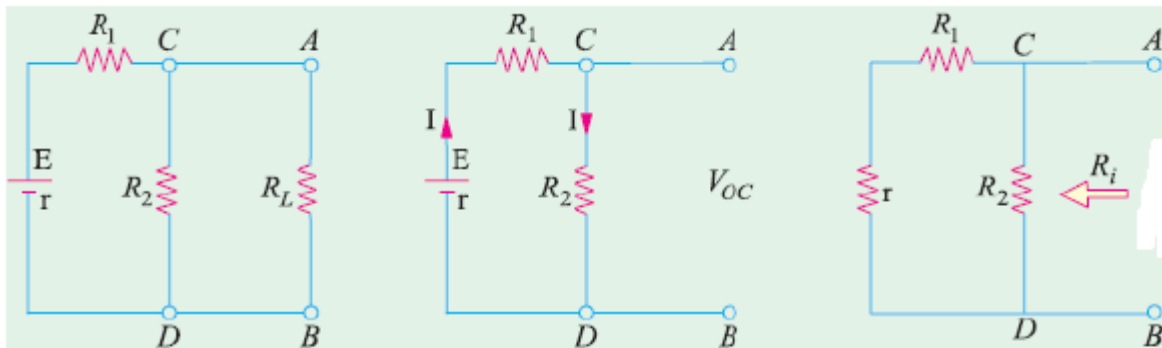


Fig.(a)

fig.(b)

fig.(c)

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

9

1. From the given circuit (fig.a), Remove  $R_L$  from the terminals A and B and redraw the circuit as shown in Fig.b.

2. Calculate the open-circuit voltage  $V_{oc}$  which appears across terminals A and B. As seen,  $V_{oc} = \text{drop across } R_2 = IR_2$  where  $I$  is the circuit current when A and B are open.

$$I = \frac{E}{R_1 + R_2 + r} \quad \therefore V_{oc} = IR_2 = \frac{ER_2}{R_1 + R_2 + r} \quad [r \text{ is the internal resistance of battery}]$$

It is also called 'Thevenin voltage'  $V_{th}$ .

3. Now, imagine the battery to be removed from the circuit, leaving its internal resistance  $r$  behind and redraw the circuit, as shown in Fig.(c). When viewed inwards from terminals A and B, the equivalent resistance is given as,


$$R = R_2 \parallel (R_1 + r) = \frac{R_2(R_1 + r)}{R_2 + (R_1 + r)}$$

This is called Thevenin's equivalent resistance  $R_{th}$ .

4. Connect  $R_L$  back across terminals A and B (fig.d) from where it was temporarily removed earlier.

Current flowing through  $R_L$  is given by

$$I = \frac{V_{th}}{R_{th} + R_L}$$


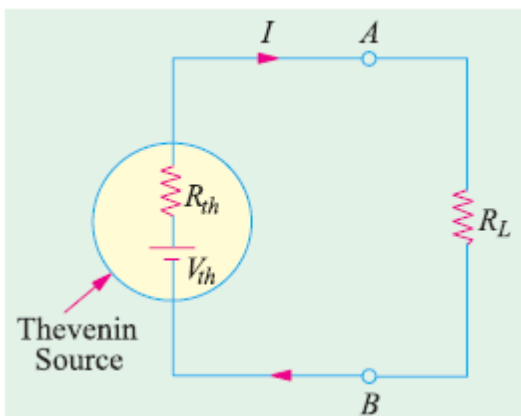


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

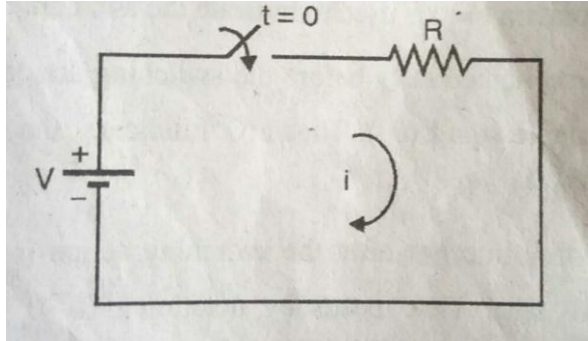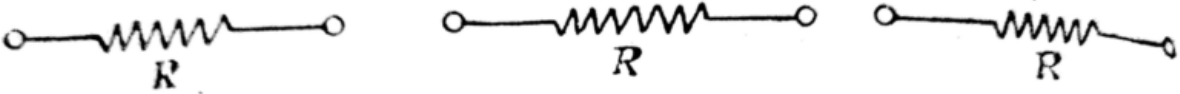
Q. No.	Sub Q. N.	Answers	Marking Scheme
3		Attempt any THREE of the following :	12- Total Marks
	a)	<p><b>Explain the concept of initial and final conditions in switching circuits for elements R and L.</b></p> <p><b>Ans:</b> Concept of Initial and final condition in switching circuits for R: Consider a resistor is connected to a voltage source, using a switch as shown in fig below</p>  <p>The switch is closed at time <math>t = 0</math>, so we get <math>V = iR</math> which is time independent equation. Here current changes as per voltage without any time delay. There is no change in the value of resistor <math>R</math>, it remains same for initial condition and final condition.</p>  <p>Initial condition                      equivalent circuit at <math>t=0+</math>                      equivalent circuit at <math>t = \infty</math></p>	<p>4M</p> <p>2M for resistance</p> <p>2M for inductance</p>
		<p><b>Concept of Initial and final condition in switching circuits for L:</b></p> <p>Consider a inductor is connected to voltage source as shown in fig below:</p>	

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network


Subject Code: 22330

Model Answer

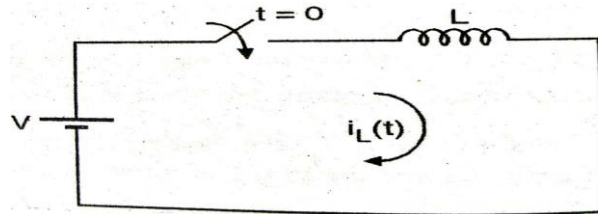

The property of inductor is to oppose any change in current. So the current through an inductor cannot change instantaneously. There are 2 cases.

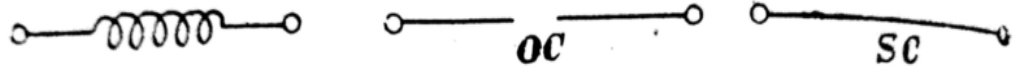
- i) If no initial current is passing through inductor, then at  $t = 0+$ , it acts as open circuit. The final condition is given by the equation  $v_L = L di/dt$ .  
At  $t = \infty$ , it acts as short circuit.



Initial condition                      equivalent circuit at  $t=0+$       equivalent circuit at  $t = \infty$

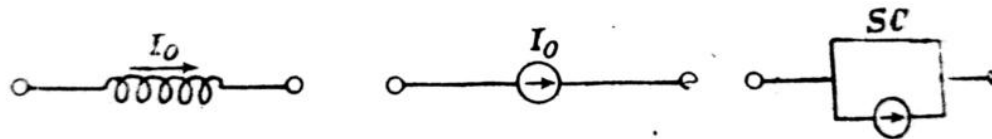- ii) If initial current is passing through inductor, then at  $t = 0+$ , it acts as constant current source of value  $I_0$ .

At  $t = \infty$ , (final condition), the inductor acts as current source of value  $I_0$  in parallel with short circuit. ( $I_0$  is the current in inductor just before switching)



Initial condition                      equivalent circuit at  $t=0+$       equivalent circuit at  $t = \infty$

b) Derive an expression for resonant frequency of series RLC circuit.

4M



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

12
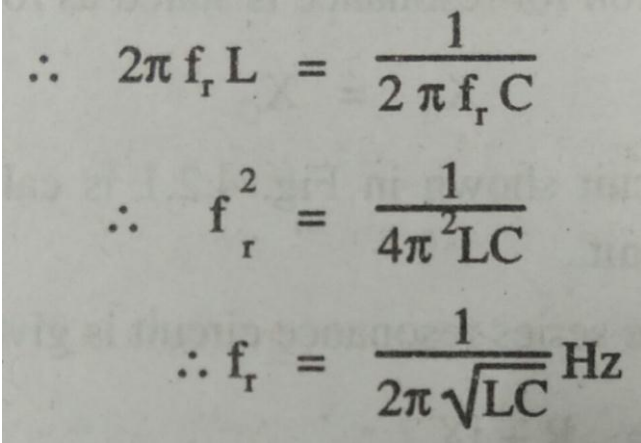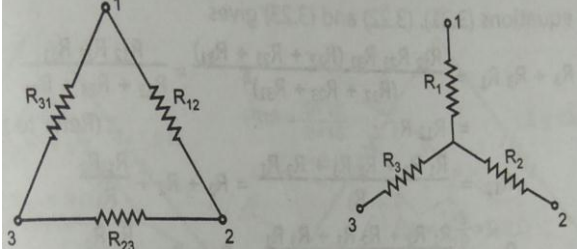
<p><b>Ans:</b></p>	<p>At resonance frequency in RLC series circuit, we have inductive reactance is equal to capacitive reactance i.e.</p> $X_L = X_C$ <p>As <math>X_L = 2\pi f_r L</math> and <math>X_C = 1/2\pi f_r C</math>, we can write</p>  <p>Where <math>f_r</math> is the resonant frequency in RLC series circuit.</p>	<p><b>4 M</b></p>
<p><b>c)</b></p>	<p><b>Derive an expression for delta to star transformation.</b></p>	<p><b>4M</b></p>
<p><b>Ans:</b></p>	 <p>Equivalent delta and star network</p> <p>For delta network the resistance between the terminals 1 and 2 consists of <math>R_{12}</math> in parallel with <math>(R_{23} + R_{31})</math>. Hence, the resistance between the terminals 1 and 2 is</p>	<p><b>1M</b></p>



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

13

$$= \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}}$$

In case of star network the resistance between the terminals 1 and 2 is  $=R_1+R_2$ , so we get

$$R_1 + R_2 = \frac{R_{12} (R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \text{---i)}$$

$$R_2 + R_3 = \frac{R_{23} (R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}}$$

$$R_3 + R_1 = \frac{R_{31} (R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}}$$

---ii & iii)

Subtracting equation (ii) from (i), we get

$$R_1 - R_3 = \frac{R_{12} R_{23} + R_{12} R_{31} - R_{23} R_{31} - R_{23} R_{12}}{R_{12} + R_{23} + R_{31}}$$

$$R_1 - R_3 = \frac{R_{12} R_{31} - R_{23} R_{31}}{R_{12} + R_{23} + R_{31}} \quad \text{---iv)}$$

1M

1M




WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

14

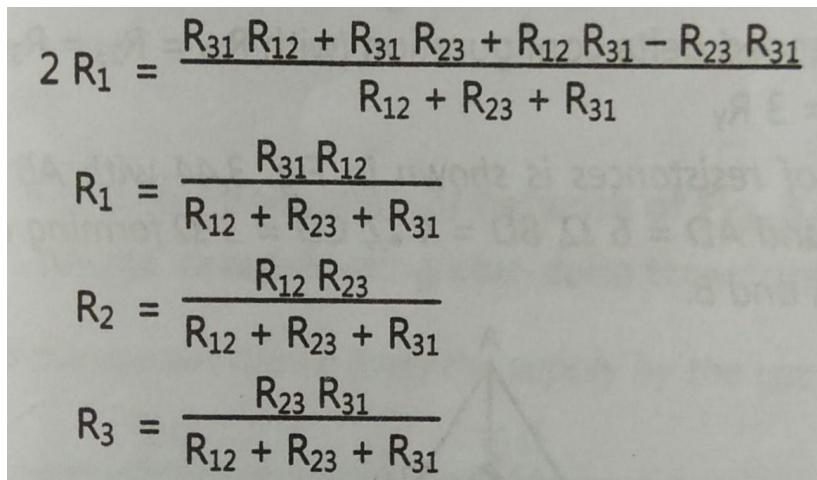	<p>Adding equations (iii) and( iv),we have</p>  $2 R_1 = \frac{R_{31} R_{12} + R_{31} R_{23} + R_{12} R_{31} - R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$ $R_1 = \frac{R_{31} R_{12}}{R_{12} + R_{23} + R_{31}}$ $R_2 = \frac{R_{12} R_{23}}{R_{12} + R_{23} + R_{31}}$ $R_3 = \frac{R_{23} R_{31}}{R_{12} + R_{23} + R_{31}}$	<p><b>1M</b></p>
<p>d)</p>	<p><b>State super position theorem. Write steps to find current in an element using super position theorem.</b></p>	<p><b>4M</b></p>
<p><b>Ans:</b></p>	<p>Statement of superposition theorem: In any linear network containing two or more sources, the current in any element is equal to algebraic sum of the current caused by individual source acting alone, while the other sources are replaced for the time being by resistances equal to their internal resistances.</p> <p>Steps to find current using superposition theorem:</p> <ol style="list-style-type: none"> <li>1. Select any one energy source.</li> <li>2. Replace all other energy sources i.e. voltage source by short circuit and current source by open circuit.</li> <li>3. Calculate voltage drop and branch current due to selected energy source.</li> <li>4. Repeat steps 1,2,3 for each source individually.</li> <li>5. Add algebraically the voltage drops and branch currents to obtain combined effect of all sources.</li> </ol>	<p><b>2M – statement</b></p> <p><b>2M for steps</b></p>





WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

15

Q. No.	Sub Q. N.	Answers	Marking Scheme
4		Attempt any THREE of the following :	12- Total Marks
	(a)	A series combination of resistance 100 ohm and capacitance 50 $\mu$ f is connected in series to a 230 V, 50HZ supply. Calculate  (i) Capacitive reactance (ii) Current (iii) Power factor (iv) Power consumed	4M
	Ans:	Solution: For RC series circuit	1M  1M  1M



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

16

	<p>Given <math>R=100 \Omega</math>, <math>C=50 \mu\text{f}</math>, <math>V=230\text{V}</math>, <math>f=50\text{Hz}</math></p> <p>(i) Capacitive Reactance</p> $X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}} = \underline{\underline{63.66 \Omega}}$ <p>(ii) Current</p> $I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + X_c^2}} = \frac{230}{\sqrt{(100)^2 + (63.66)^2}}$ $= \frac{230}{118.54} = \underline{\underline{1.94 \text{ A}}}$ <p>(iii) Power factor</p> $\cos \phi = \frac{R}{Z} = \frac{100}{118.54} = \underline{\underline{0.8435}} \text{ leading}$ <p>(iv) Power consumed</p> $P = V I \cos \phi = 230 \times 1.94 \times 0.8435$ $= \underline{\underline{376.36 \text{ W}}}$	<p>1M</p>
<p>(b)</p>	<p>Two impedances given by <math>Z_1 = 10 + j5</math> and <math>Z_2 = 8 + j9</math> are joined in parallel and connected across a voltage of <math>V = 200 + j0</math>. Calculate the circuit current and branch currents. Draw the vector diagram.</p>	<p>4M</p>
<p>Ans:</p>	<p>Solution:</p> <p>Given, <math>Z_1=10+j5</math>, <math>Z_2=8+j9</math>, <math>V=200+j0</math></p>	



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

17

Given:  $Z_1 = 10 + j5$ ,  $Z_2 = 8 + j9$  and  $v = 200 \angle 0^\circ$

To find circuit current first we have to calculate total admittance

(a) Total admittance

$$\begin{aligned} Y &= Y_1 + Y_2 = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{10 + j5} + \frac{1}{8 + j9} \\ &= \frac{1}{11.18 \angle 26.56^\circ} + \frac{1}{12.04 \angle 48.36^\circ} \\ &= 0.089 \angle -26.56^\circ + 0.083 \angle -48.36^\circ \\ &= (0.08 - 0.04j) + (0.06 - 0.06j) \\ &= 0.14 - 0.1j \\ &= \underline{0.17 \angle -35.53^\circ} \end{aligned}$$

1M

(b) Circuit current,  $I = v \times Y$

$$\begin{aligned} &= (200 \angle 0^\circ) (0.17 \angle -35.53^\circ) \\ &= \underline{34 \angle -35.53^\circ} \text{ A} \end{aligned}$$

1M

(c) Branch current

$$\begin{aligned} I_1 &= v \times Y_1 \\ &= (200 \angle 0^\circ) (0.089 \angle -26.56^\circ) \\ &= \underline{17.8 \angle -26.56^\circ} \text{ A} \end{aligned}$$


1M

$$I_2 = v \times Y_2$$

$$\begin{aligned} &= (200 \angle 0^\circ) (0.083 \angle -48.36^\circ) \\ &= \underline{16.6 \angle -48.36^\circ} \text{ A} \end{aligned}$$

1M

(d) Vector Diagram

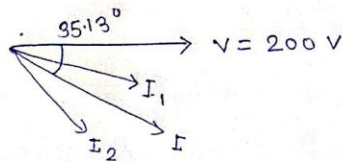

(c) An a.c series circuit has resistance of 10ohm, inductance of 0.1H and capacitance of 10 $\mu$ f, voltage applied to circuit is 200V. find

4M

- (i) Resonant frequency
- (ii) Current at resonance
- (iii) Power at resonance



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

18

Ans:	Solution: For RLC series circuit	2M
	Given: $R = 10 \Omega$ , $L = 0.1 \text{ H}$ , $C = 10 \mu\text{F}$ , $V = 200 \text{ V}$	
	(i) Resonant frequency $f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 10 \times 10^{-6}}}$ $= 159.13 \text{ Hz}$	1M
	(ii) current at resonance, $I = \frac{V}{Z}$ $= \frac{V}{R} = \frac{200}{10} = 20 \text{ A}$	1M
	(iii) Power at resonance, $P = VI \cos \phi$ $= 200 \times 20 \times 1 = 4000 \text{ W}$ $= 4 \text{ kW}$	
(d)	Use mesh analysis to calculate ammeter current in Fig No. 1	4M


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

19

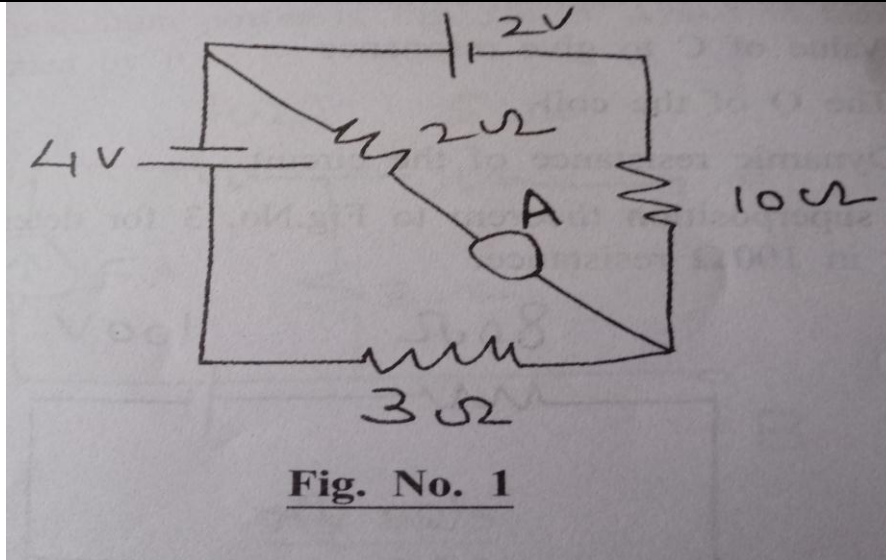

Ans:

(a) Applying mesh analysis to loop ABCA, we have  
 $-2 - 10I_1 - 2(I_1 - I_2) = 0$   
 $\therefore -2 - 12I_1 + 2I_2 = 0$   
 $\therefore -6I_1 + I_2 = 1 \quad \text{--- (i)}$

1M

(b) Applying mesh analysis to loop ACDB, we have  
 $-2(I_2 - I_1) - 3I_2 - 4 = 0$   
 $\therefore -5I_2 + 2I_1 - 4 = 0$   
 $\therefore 2I_1 - 5I_2 = 4 \quad \text{--- (ii)}$

1M

Multiplying eq<sup>n</sup> (ii) by 3 we get,  
 $6I_1 - 15I_2 = 12 \quad \text{--- (iii)}$

1/2M

Adding eq<sup>n</sup> (i) & (iii) we get  
 $-14I_2 = 13$   
 $\therefore I_2 = -13/14 = -0.92 \text{ A}$

1/2M

From eq<sup>n</sup> (i)  $-6I_1 + (-0.92) = 1$   
 $\therefore -6I_1 = 1.92$   
 $\therefore I_1 = -0.32 \text{ A}$

$\therefore$  Current in ammeter is  $I_1 - I_2 = -0.32 - (-0.92)$   
 $= -0.32 + 0.92$   
 $= \underline{0.6 \text{ A (cto A)}}$

1M

WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

20
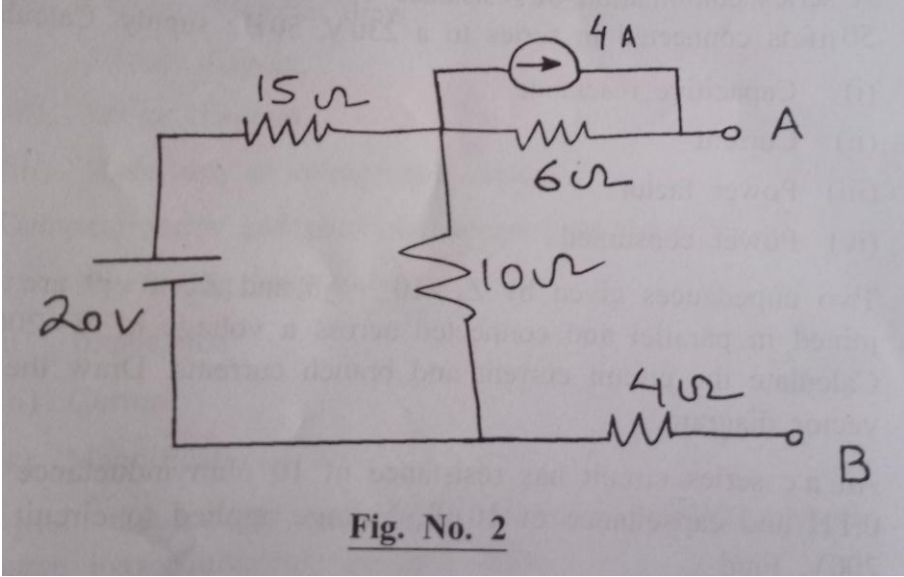
<p>(e)</p>	<p>Find the Norton equivalent resistance for the network shown in Fig No. 2</p>  <p style="text-align: center;"><u>Fig. No. 2</u></p>	<p>4M</p>
<p>Ans:</p>	<p>Solution: To find Norton's equivalent resistance removing voltage source and current source. Voltage source is replaced by short circuit and current source is replaced by open circuit so, we get circuit as</p>	<p>Diagram :1M  R<sub>N</sub> calculation :3M</p>



WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

21

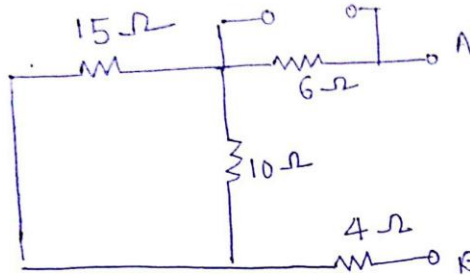

Tracing circuit from A & B, we have  $15\Omega$  &  $10\Omega$  resistor in parallel.

$$\therefore \text{Its equivalent resistance } R_{eq} = \frac{15 \times 10}{15 + 10} = 6\Omega$$

Now  $6\Omega$ ,  $6\Omega$  &  $4\Omega$  resistor are in series,

$$\therefore \text{we have } R_s = 6 + 6 + 4 = 16\Omega$$

$$\therefore \text{Norton's equivalent resistance } \underline{R_N = 16\Omega}$$

Q. No.	Sub Q. N.	Answers	Marking Scheme
5.		Attempt any TWO of the following:	12- Total Marks
	a)	<p>A coil of resistance 20 ohm and inductance of <math>200\mu\text{H}</math> is in parallel with variable capacitor. This combination is in series with a resistance of 8000 ohm. The voltage of the supply is 200 V and at frequency of <math>10^6</math> Hz. Calculate</p> <p>(i) Value of C to give resonance                      (ii) The Q of the coil                      (iii) Dynamic resistance of the circuit.</p>	6M



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

22

Ans:

Ans :→

$$\begin{aligned} \textcircled{1} \text{ Inductive Reactance } X_L &= 2\pi fL \\ &= 2 \times \pi \times 10^6 \times 200 \times 10^{-6} \\ &= 1256 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{2} \text{ Impedance } Z &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{20^2 + (1256)^2} \\ Z &= 1256.16 \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{3} \quad Z_L^2 &= L/C \quad \text{at parallel Resonance} \\ \text{Value of } C \text{ at Resonance} \rightarrow C &= \frac{L}{Z_L^2} = \frac{200 \times 10^{-6}}{(1256.16)^2} = 125.5 \times 10^{-12} \text{ F} \\ &= 125.5 \text{ pF} \end{aligned}$$

$$\begin{aligned} \textcircled{4} \text{ Q of coil} &= \frac{2\pi f r L}{R} \\ &= \frac{2\pi \times 10^6 \times 200 \times 10^{-6}}{20} = 62.8 \end{aligned}$$

⑤ Dynamic Resistance of coil circuit

$$\begin{aligned} Z_r &= \frac{L}{CR} \\ Z_r &= \frac{200 \times 10^{-6}}{125.6 \times 10^{-12} \times 20} = 78957 \Omega \end{aligned}$$

i) Value of C -2 Marks,

ii) Q of coil -2 Marks

iii) Dynamic Resistance -2 Marks





WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

23

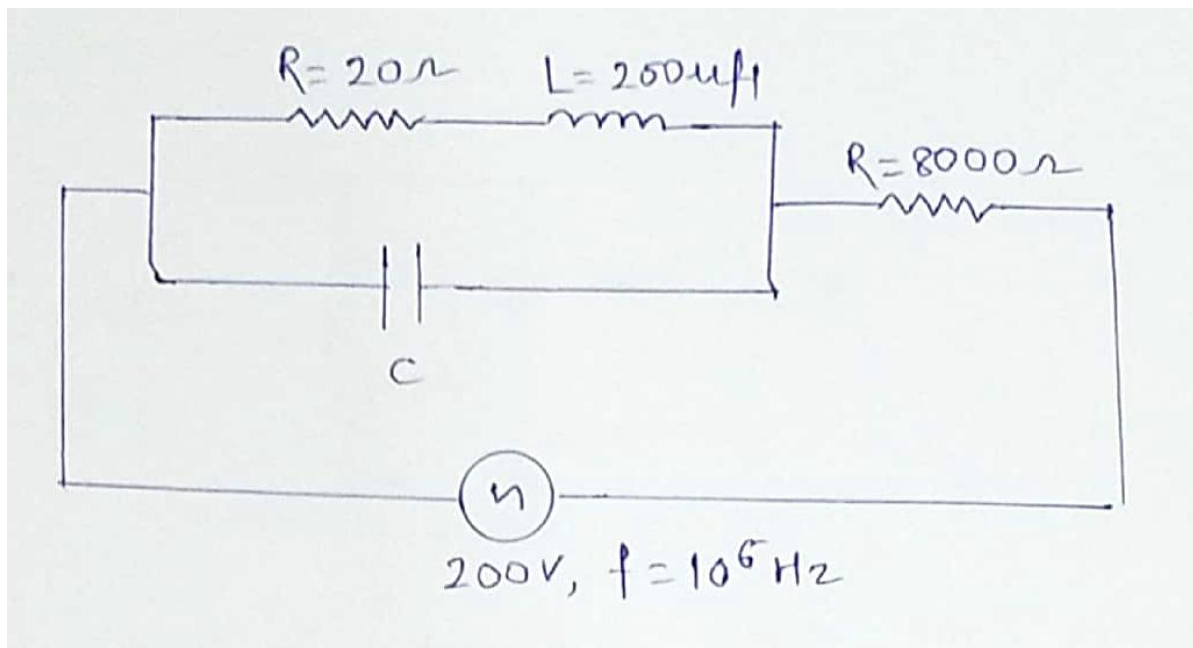

b) Apply superposition theorem to Fig No. 3 for determining the current in 100  $\Omega$  resistance.

6M

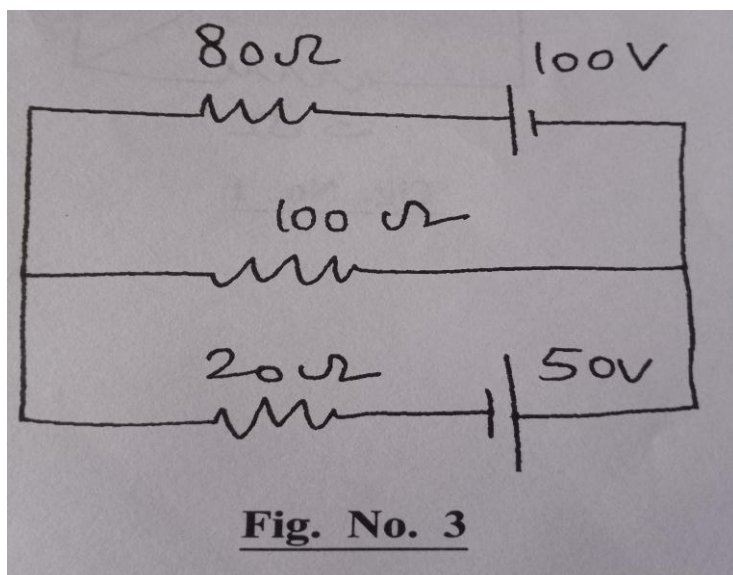


Fig. No. 3

WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code: 22330


Model Answer

Ans:

Ans :-

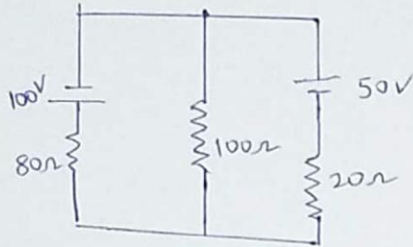

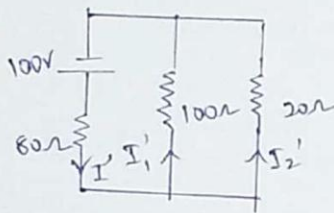Step 1:- consider only 100V source & short 50V supply



Total Resistance across supply  


$$= 80 + \frac{100 \times 20}{100 + 20} = 96.66$$

$$I' = \frac{100}{96.66} = 1.034$$

current in  $\frac{100\Omega}{20\Omega}$  resistor =  $\frac{20}{120} \times 1.034 = 0.172$

$$I_1' = 0.172A$$

Step 2:- consider only 50V source

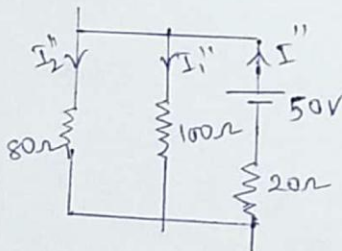

Total Resistance across supply  

$$= 20 + \frac{80 \times 100}{80 + 100} = 64.44$$

$$I'' = \frac{50}{64.44} = 0.7759$$

current in 100Ω resistor =  $\frac{80}{180} \times 0.7759 = 0.3448$

$$I_1'' = 0.3448$$

Therefore current 100Ω resistor

$$I_1 = I_1'' - I_1' = 0.3448 - 0.172 = 0.1728A$$

Step 1 -  
2.5  
Marks



Step 2 -  
2.5 Marks  
Final  
current 1  
Mark

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer
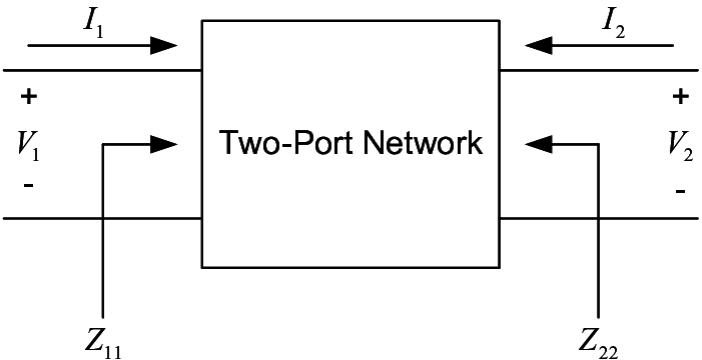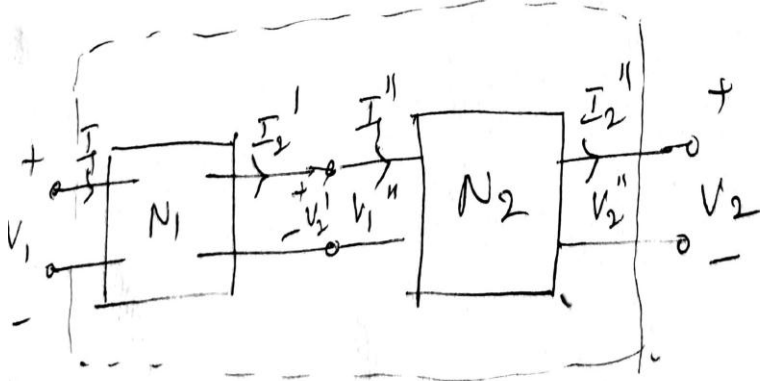
<p>c)</p>	<p>Draw the two port network and determine the indicated parameters for the following configuration</p> <p>(i) Cascade configuration (ABCD parameter) (ii) Series configuration (iii) Parallel configuration</p>	<p>6M</p>
<p>Ans:</p>	 <p>i) Cascade Configuration</p>  <p>2 Nws. <math>N_1</math> and <math>N_2</math> connected in <u>cascade</u></p>	<p>Each configuration : 1M</p> <p>Equation for parameter : 1M</p>

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330


Model Answer

A, B, C, D are the parameters of cascade network, then

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_1 & B_1 \\ C_1 & D_1 \end{bmatrix} \begin{bmatrix} A_2 & B_2 \\ C_2 & D_2 \end{bmatrix}$$

for cascade configuration, ABCD parameters has to be multiplied.

ii) Series Configuration

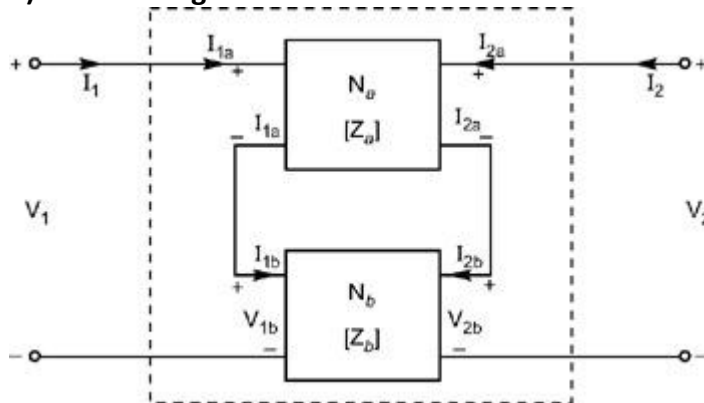

ii) Series configuration (Refer diagram for the same)

$$Z_{11} = Z_{11a} + Z_{11b}$$

$$Z_{12} = Z_{12a} + Z_{12b}$$

$$Z_{21} = Z_{21a} + Z_{21b}$$

$$Z_{22} = Z_{22a} + Z_{22b}$$

$$[Z] = [Z_a] + [Z_b]$$

iii) Parallel Configuration


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

27

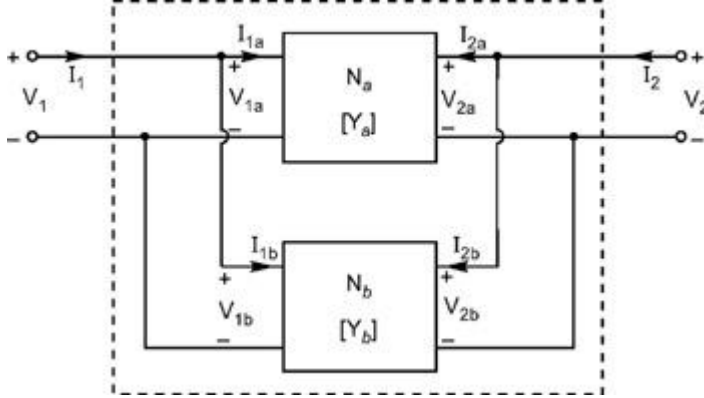

iii) Parallel configuration (Refer diagram for the same) -

$$I_1 = (Y_{11a} + Y_{11b})V_1 + (Y_{12a} + Y_{12b})V_2$$

$$I_2 = (Y_{21a} + Y_{21b})V_1 + (Y_{22a} + Y_{22b})V_2$$

that is  $Y$  parameters for combined network can be written as

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

where  $Y_{11} = Y_{11a} + Y_{11b}$

$$Y_{12} = Y_{12a} + Y_{12b}$$

$$Y_{21} = Y_{21a} + Y_{21b}$$

$$Y_{22} = Y_{22a} + Y_{22b}$$

Q. No.	Sub Q. N.	Answers	Marking Scheme
6.		Attempt any TWO of the following :	12- Total

WINTER-19 EXAMINATION


Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

28

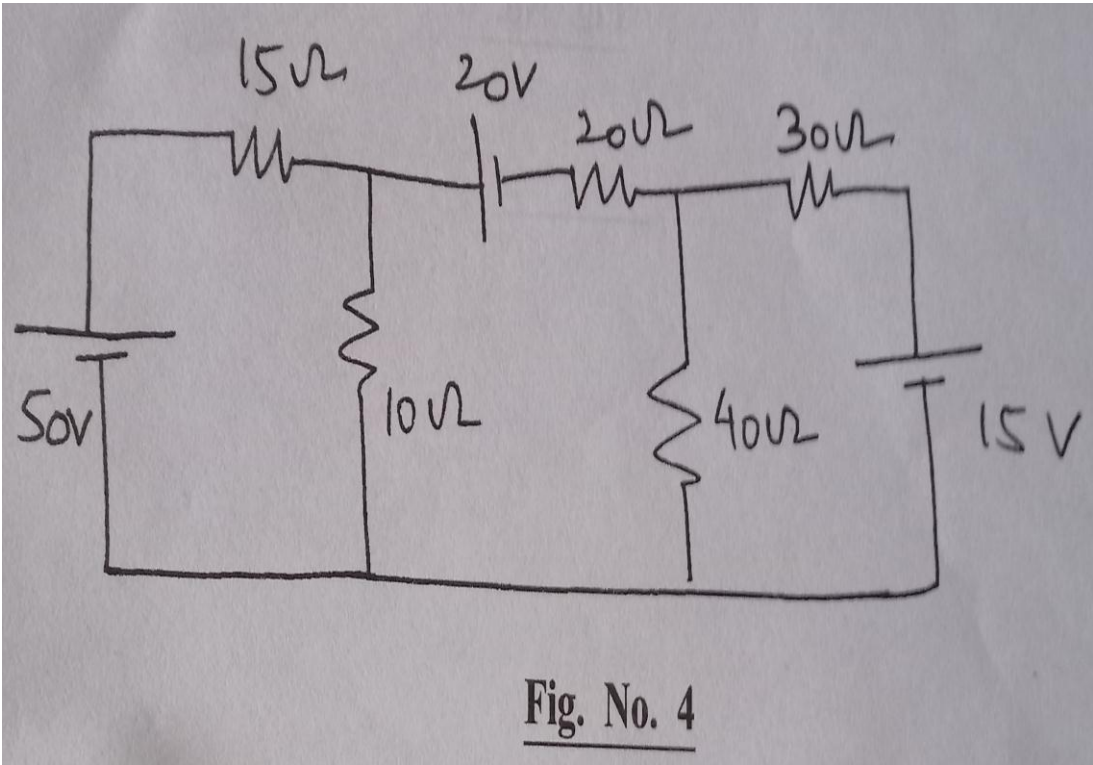		Marks
a)	<p>Find current in <math>40\ \Omega</math> and <math>10\ \Omega</math> in Fig no. 4 node voltage analysis method.</p>  <p><u>Fig. No. 4</u></p>	6M

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network


Subject Code:

22330

Model Answer

29

Ans:

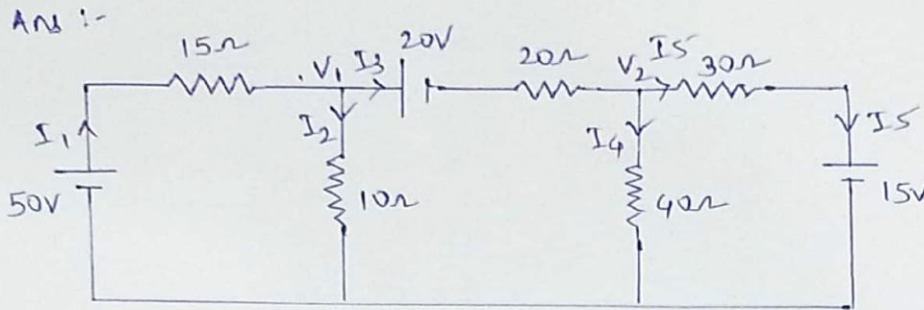

Applying KCL at nodes  $V_1$  &  $V_2$ ,

$$I_1 = I_2 + I_3 \quad \rightarrow \textcircled{1}$$

$$I_3 = I_4 + I_5 \quad \rightarrow \textcircled{2}$$

for first equation

$$I_1 = I_2 + I_3$$

$$\left( \frac{50 - V_1}{15} \right) = \frac{V_1}{10} + \left( \frac{V_1 - 20 - V_2}{20} \right)$$

$$\left( \frac{50 - V_1}{15} \right) = \frac{2V_1 + V_1 - 20 - V_2}{20}$$

$$\frac{50 - V_1}{15} = \frac{3V_1 - 20 - V_2}{20}$$

$$20(50 - V_1) = 15(3V_1 - 20 - V_2)$$

$$1000 - 20V_1 = 45V_1 - 300 - 15V_2$$

$$1300 = 65V_1 - 15V_2 \quad \rightarrow \textcircled{3}$$

for second equation

$$I_3 = I_4 + I_5$$

$$\left( \frac{V_1 - 20 - V_2}{20} \right) = \frac{V_2}{40} + \left( \frac{V_2 - 15}{30} \right)$$

V1 - 2  
marks, V2  
- 2 Marks,

I through  
40 ohms -  
1 Mark,

I through  
30 ohm -  
1 Mark



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330

Model Answer

30

$$\frac{V_1 - V_2 - 20}{20} - \frac{V_2}{40} - \frac{V_2 - 15}{30} = 0$$

$$\frac{6V_1 - 6V_2 - 120 - 3V_2 - 4V_2 + 60}{120} = 0$$

$$6V_1 - 13V_2 - 60 = 0$$

$$6V_1 - 13V_2 = 60 \rightarrow (4)$$

By solving (3) & (4) we get  
Multiplying (3) by 13 & (4) by 15, we get

$$V_1 = 21.19$$

$$V_2 = 5.17$$

$$I_4 = \frac{V_2}{40} = \frac{5.17}{40} = 0.13 \text{ A}$$

$$I_5 = \frac{V_2 - 15}{30} = \frac{5.17 - 15}{30} = -0.327 \text{ A}$$

b) Find the value of resistance to be connected across AB so as to consume maximum power in Fig No. 5. Also find maximum power consumed by it.

6M





WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

31

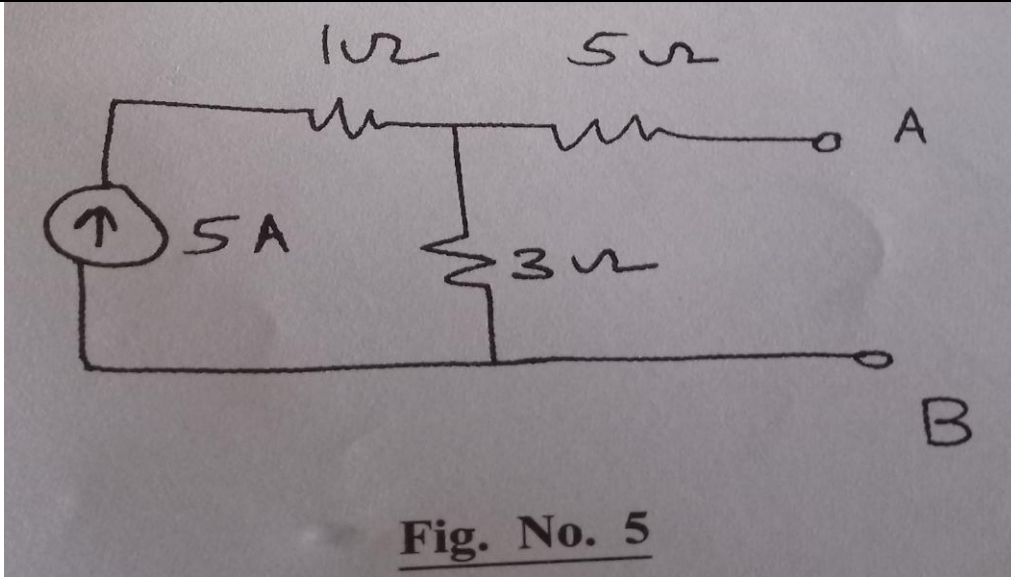


Fig. No. 5

WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code: 22330


Model Answer

32

Ans:

Ans :-  
Maximum Power will be transferred when  
 $R_{TH} = R_L$ , so find out  $R_{TH}$  first.


① To find  $R_{TH}$ , open SA source

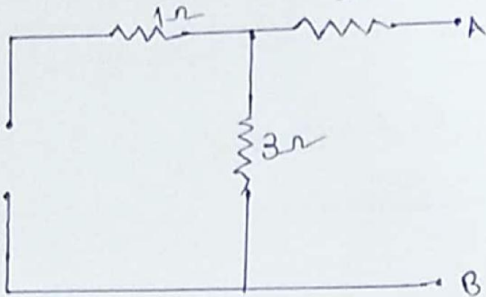

$R_{TH} = 3 + 5 = 8\Omega$

$R_L = 8\Omega = R_{TH}$  to transfer maximum power.

② To find  $V_{oc}$ .

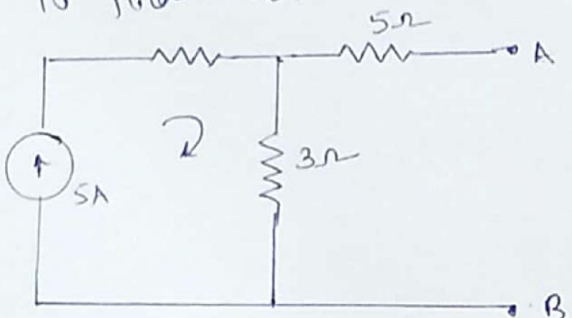

current through  $3\Omega = 5 \times 3 = 15$

$\therefore V_{oc} = 5 \times 3 = 15$

Maximum Power =  $\frac{V_{oc}^2}{4R_L} = \frac{15^2}{4 \times 8} = 7.03125 \text{ W}$ .

Rth -2  
Marks,

Voc -  
2Marks,

Power -  
2Marks

c) Find Z parameters for the network shown in Fig No. 6

6M



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

33

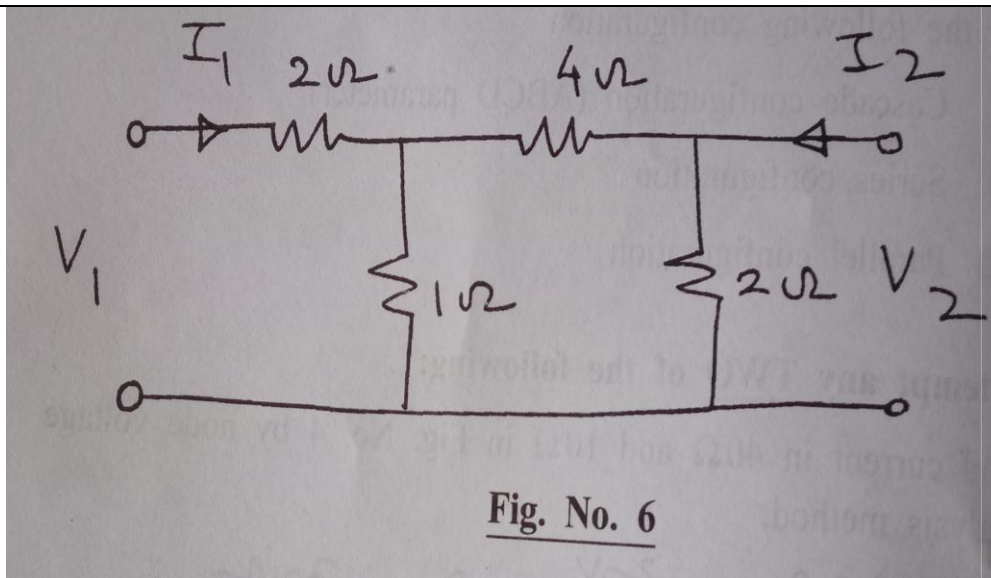


Fig. No. 6

Ans:

Z11-2  
Marks,  
Z12-  
1Mark,  
Z21 -  
2Marks,  
Z22-  
1Mark


WINTER-19 EXAMINATION

Subject Name: Electric circuits and network


Subject Code: 22330

Model Answer

Ans :-

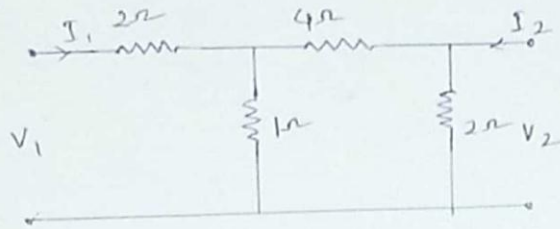

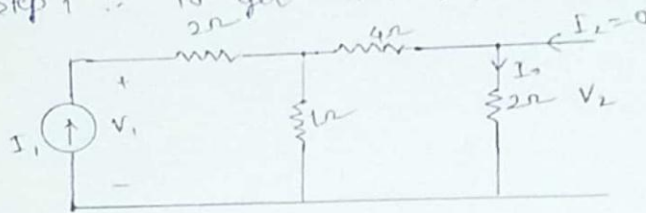Step 1 :- To get  $Z_{11}$  &  $Z_{21}$ , consider the circuit as




$$Z_{11} = \frac{V_1}{I_1} = 2 + j11(4+2)$$

$$= 2 + \frac{1 \times 6}{1+6} = 2 + \frac{6}{7} = 2.85$$

$$I_0 = \frac{1}{2} I_1$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{2 \left( \frac{1}{7} I_1 \right)}{I_1} = \frac{2}{7} \Omega = 0.28$$

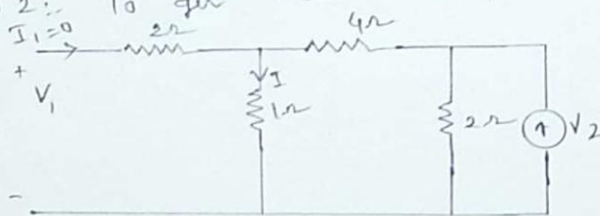Step 2 :- To get  $Z_{22}$  &  $Z_{12}$ , consider the circuit as



$$Z_{22} = \frac{V_2}{I_2} = 2 \parallel (4+1) = \frac{2 \times 5}{2+5} = \frac{10}{7} = 1.44$$

$$I = \frac{2}{2+5} \times I_2 = \frac{2}{7} I_2 \quad V_1 = 1 \times I = 1 \times \frac{2}{7} I_2 = \frac{2}{7} I_2$$

$$Z_{12} = \frac{V_1}{I_2} = \frac{2}{7} I_2 \times \frac{1}{I_2} = \frac{2}{7} = 0.28$$



WINTER-19 EXAMINATION

Subject Name: Electric circuits and network

Subject Code:

22330

Model Answer

35

$$Z = \begin{bmatrix} 2.85 & 0.28 \\ 0.28 & 1.44 \end{bmatrix} \Omega$$